

x_1x_2		00	01	11	10
y	a	(a), 0	(a), 0	(a), 0	b, -
	b	(b), 1	a, -	(b), 1	(b), 1

- (d) When the input is 01, the output is 0. When the input is 10, the output is 1. Whenever the input assumes one of the other two combinations, the output retains its previous value.

9.4

$$Y_1 = x_1x_2 + x_1y'_2 + x'_2y_1$$

x_1x_2		00	01	11	10
y_1y_2	00	(00)	01	11	10
	01	00	01	11	(01)
	11	(11)	01	(11)	10
	10	11	01	11	(10)

Transition Table

$$Y_2 = x_2 + x_1y'_1y'_2 + x'_1y_1$$

x_1x_2		00	01	11	10
y_1y_2	00	0	1	1	0
	01	0	1	1	0
	11	1	1	1	1
	10	1	1	1	1




Output Map

$$z = x_2 + y_1$$


y_1y_2		00	01	11	10
$a = 00$	a	(a), 0	b, 1	c, 1	d, 0
	b = 01	a, 0	(b), 1	c, 1	(b), 0
	c = 11	(c), 1	b, 1	(c), 1	d, 1
	d = 10	c, 1	b, 1	c, 1	(d), 1

Flow Table


9.5

  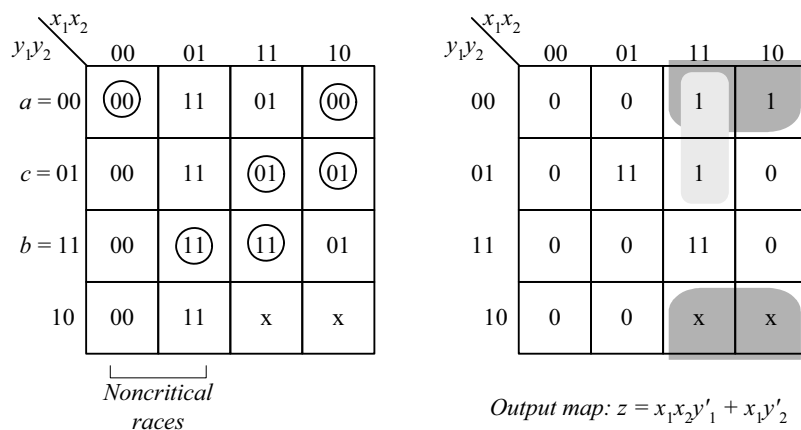


9.6

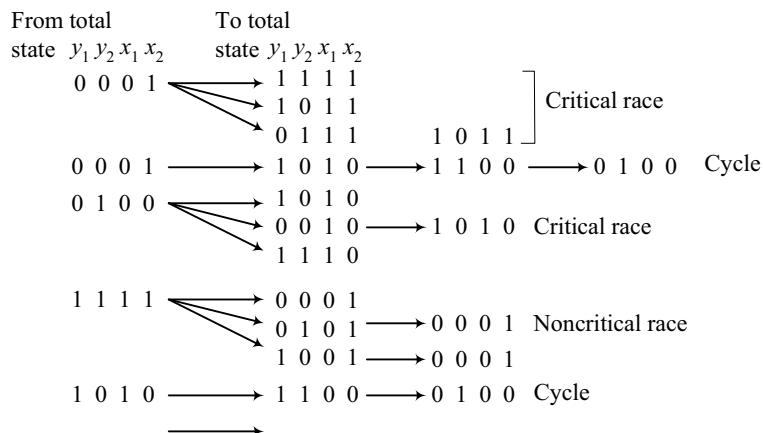

 - 9.7** When all the inputs are equal to 1, both outputs are equal to 1. (See Fig. 9.11). Going from $SR = 11$ to $SR = 00$ when $C = 1$ produces an unstable output.



 - 9.8** When $C = 1$ and $J = K = 1$, the outputs complement and again repeat complementing as long as $C = 1$.



- 9.9 (a)**

$$\begin{aligned} S_1 &= x'_1 & R_1 &= y'_2 \\ S_2 &= x'_1 y'_1 & R_2 &= x'_2 \end{aligned}$$

$$\begin{aligned} Y_1 &= S_1 + R_1 y_1 = x_1 + y_1 y'_2 \\ Y_2 &= S_2 + R_2 y_2 = x_1 + y_1 + x'_2 y_2 \end{aligned}$$

$$Q = Y_2$$

- (b)**

$y_1 y_2 \backslash x_1 x_2$	00	01	11	10
00	00	00	11	11
01	01	00	11	11
11	01	01	11	11
10	00	11	11	11

Transition table

$y_1 y_2 \backslash x_1 x_2$	00	01	11	10
00	0	0	1	1
01	1	0	1	1
11	1	1	1	1
10	1	1	1	1

Output map

9.10

$$Y = x_1x'_2 + (x_1 + x'_2)y = S + R'y$$

x_1x_2		x_1			
		00	01	11	10
y	0	0	0	0	0
	1	1	1	1	1

Transition map



y	Y	S	R
0	0	0	x
0	1	1	0
1	0	0	1
1	1	x	0

x_1x_2		x_1			
		00	01	11	10
y	0	0	0	0	0
	1	1	1	1	1

$$S = x_1x'_2$$

x_1x_2		x_1			
		00	01	11	10
y	0	0	0	0	0
	1	1	1	1	1

$$R = x'_1x_2$$

  


9.11 Use solution of Prob. 9.4 transition table.

x_1x_2		y_1y_2			
		00	01	11	10
00	0	0	0	1	1
	1	0	0	1	0
01	0	x	0	x	x
	1	x	0	x	x

$$S_1 = x_1x_2 + x_2y'_2$$

x_1x_2		y_1y_2			
		00	01	11	10
00	0	x	x	0	0
	1	x	x	0	x
01	0	0	1	0	0
	1	0	1	0	0

$$R_1 = x'_1x_2$$

 

The circuit may be drawn as in Fig. 9.38(b) or Fig. 9.46. It will require 6 NAND gates for the inputs to the latches, 4 NAND gates for the two latches, and one NAND gate for the out put $z = x_2 + y_1 = (x_2'y_1)'$.

9.12

		x_1x_2				
		00	01	11	10	
a	(a),00	b,-	-,-	c,-		Initial state
b	a,-	(b),00	d,-	-,-		No change of output
c	a,-	-,-	g,-	(c),00		No change of output
d	-,-	f,-	(d),10	e,-		x_1x_2 from 01 to 11 [Condition (c)]
e	a,-	-,-	g,-	(e),10		No change of output
f	a,-	(f),10	g,-	-,-		No change of output
g	-,-	j,-	(g),01	h,-		x_1x_2 from 10 to 11 [Condition (b)]
h	a,-	-,-	g,-	(h),01		No change of output
j	a,-	(j),01	d,-	-,-		No change of output

9.13

		Switch input	Output light (red = 1)	
State	x_1x_2	z	Comments	
a	0 0	0	No train in intersection	
b	0 1	1	Train turns on x_2 after state a	
c	0 0	1	Train between two switches	
d	1 0	1	Train turns on x_1 after state c	
e	1 0	1	Train trains on x_1 after state a	
f	0 0	1	Train between two switches	
g	0 1	1	Train turns on x_2 after state f	

$z = x_2 + y_1$

$y_1 y_2$	00	01	11	10
a	(a), 0	b, -	-, -	e, -
b	c, -	(b), 1	-, -	-, -
c	(c), 1	-, -	-, -	d, -
d	a, -	-, -	-, -	(d), 1
e	f, -	-, -	-, -	(e), 1
f	(f), 1	g, -	-, -	-, -
g	a, -	(d), 1	-, -	-, -

```

graph TD
    a -- "x2=1" --> b
    a -- "x2=0" --> c
    b -- "x1=1" --> d
    c -- "x1=1" --> d
    e -- "x1=1" --> f
    f -- "x1=0" --> g
    g -- "x2=1" --> d
    
```

	a	b	c	d	e	f
b	a, c x					
c	x					
d	d, e x	a, c x	a, c x			
e	a, f x	c, f	c, f d, e x	a, f x		
f	x	c, f b g x		a, f x		
g	b g x	a, c x	a, c x		a, f x	x

$(b, c) (b, e) c, f (d, g) (e, f)$

```

graph TD
    a --- b
    a --- c
    a --- d
    b --- c
    c --- d
    c --- e
    d --- e
    e --- f
    f --- g
    
```

There are two possibilities for a four-row flow table:

(a) $(b, c) (d, g) (e, f)$ or (a) $(b, e) (c, f) (d, g)$. Continue with the solution of Prob. 9.25.

9.14

(b)

y	$x_1 x_2$	00	01	11	10
a = 0		0	0	1	0
b = 1		0	1	1	1

$Y = yx_1 + yx_2 + x_1x_2$

y	$x_1 x_2$	00	01	11	10
0		0	1	x	1
1		0	0	0	0

$z = y'(x_1 + x_2)$

9.15

	00	01	11	10
00	0	x	x	x
01	0	1	x	x
11	0	x	1	0
10	x	1	1	1

(a)

	00	01	11	10
00	0	0	x	0
01	0	0	1	1
11	x	1	1	1
10	0	1	1	0

(b)

9.16


b	$a, c\ x$ $b, d\ x$			
c	$b, d\ x$	$a, c\ x$		
d	x	x	x	
e	x	x	x	$a, e\ x$
	a	b	c	d

9.17

<i>b</i>	<i>b, c x</i> <i>d, f x</i>						
<i>c</i>	<i>b, e x</i>	<i>d, f x</i> <i>c, e x</i>					
<i>d</i>	<i>x</i>	<i>x</i>	<i>x</i>				
<i>e</i>	<i>b, c x</i> <i>d, f x</i>	<i>x</i>	<i>d, f x</i>	<i>x</i>			
<i>f</i>	<i>x</i>	<i>x</i>	<i>x</i>	<i>x</i>	<i>x</i>		
<i>g</i>	<i>x</i>	<i>x</i>	<i>x</i>	<i>x</i>	<i>x</i>	<i>x</i>	
<i>h</i>	<i>x</i>	<i>x</i>	<i>x</i>	<i>x</i>	<i>x</i>	<i>x</i>	<i>x</i>
	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>g</i>

(a, c) (b, e) (d, h) (f) (g)
See solution to Prob. 6.14 for the reduced state table.


9.18 (a)

 

- 1: (a, b) (a, e) (a, f) (a, g) (a, h)
(b, g) (b, h) (c, d) (c, h)
(d, e) (d, h) (e, f) (e, g) (e, h)
(f, g) (f, h) (g, h)

- 2, 3: (a, b) (c, d) e, f, g, h)

(b)

 

- 1: (a, e) (a, f) (b, c) (b, j) (c, d)
(d, g) (e, f) (g, h)

- 2: (a, e, f) (b, c) (b, j) (c, d)
(d, g) (g, h) (k)

- 3: (a, e, f) (b, j) (c, d) (g, h) (k)


9.19

y_1y_2 \ x_1x_2	00	01	11	10
a = 00	00	00	01	10
b = 01	00	01	01	11
c = 11	00	xx	10	11
d = 10	00	00	10	10

Transition table


y_1y_2 \ x_1x_2	00	01	11	10
00	0	1	x	x
01	0	0	0	0
11	0	x	x	0
10	x	1	1	1

Output map = z

 

$S_1 = x_1x'_2$
 $R_1 = x'_1$
 $S_2 = x_1x_2y'_1$
 $R_2 = x'_1x'_2 + x_2y_1$
 $z = x_2y'_2 + x_1y'_2$

9.20

 

Transition diagram


	00	01	11	10
0	a	g	b	f
1	c	h	d	e

Binary assignment
(Add states g and h)

	00	01	11	10
000 = a	(a)	a g	(a)	c
011 = b	a g	(b)	(b)	d
100 = c	d h	(c)	b h	(c)
111 = d	(d)	(d)	e	(d)
110 = e	f	c	(e)	c
010 = f	(f)	b	a	(f)
001 = g	a	h	b	-
101 = h	d	d	g	-

Modified flow table

9.21

 

Transition diagram

	00	01	11	10
0	a ₁	b ₁	c ₁	d ₁
1	c ₂	d ₂	a ₂	b ₂


Binary assignment

	00	01	11	10
000 = a ₁	(a ₁)	c ₂	(a ₁)	d ₁
011 = a ₂	(a ₂)	c ₁	(a ₂)	d ₂
100 = b ₁	a ₁	(b ₁)	c ₁	(b ₁)
111 = b ₂	a ₂	(b ₂)	c ₂	(b ₂)
110 = c ₁	(c ₁)	(c ₁)	(c ₁)	d ₁
010 = c ₂	(c ₂)	(c ₂)	(c ₂)	d ₂
001 = d ₁	(d ₁)	b ₂	a ₁	(d ₁)
101 = d ₂	(d ₂)	b ₁	a ₂	(d ₂)


Flow table

 9.22 $F(A, B, C, D) = \Sigma(0, 2, 6, 7, 8, 10, 12)$


$F = A'D' + AC'D' + A'BC + A'CD'$ (Note: the term $A'CD'$ is redundant)




9.23

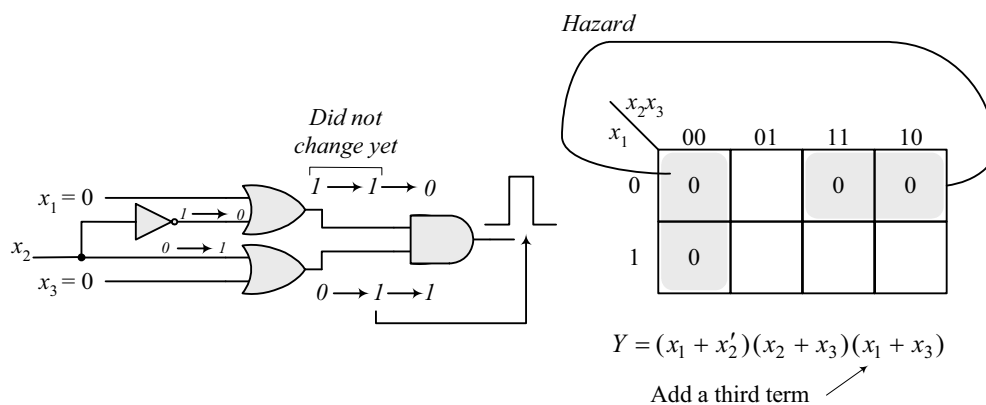

9.24

 


9.25 Continued from solution to Prob. 9.13. The four row table obtained from the compatibles (a) (b, c) (d, g) (e, f) requires three state variables because there is a critical race. Use (a) (b, e) (c, f) (d, g).

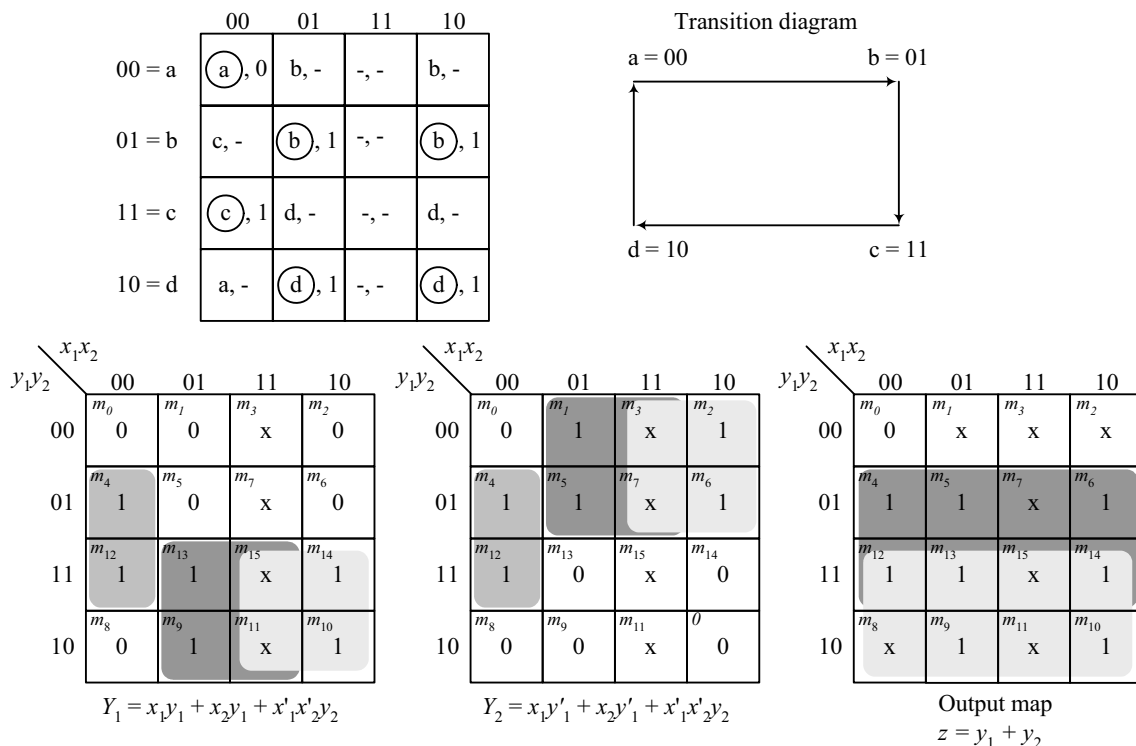

CHAPTER 10


- 10.1** Fan-out = $I_{OL}/I_{IL} = 20/2 = 10$; $I_{OH}/I_{IH} = 1/0.050 = 20$
 Power dissipation $5 \times (10 + 20)/2 = 75 \text{ mW}$ for 4 gates, $75/4 = 18.75 \text{ mW}$ per gate
 Propagation delay = 3 ns Noise margin = $2.7 - 2 = 0.7$ or $0.8 - 0.5 = 0.3 \text{ V}$

10.2

 

(a) $V_o = 90/(640 + 90) \times 3.6 + 0.7 \times 640/(640 + 90) = 0.444 + 0.614 = 1.058 \text{ V}$


(b)

 

$I_{CS}/h_{FE} = (3.6 - 0.2)/640/20 = 0.266 \text{ mA}$
 For saturation: $I_B = (V_i - 0.7)/450 \geq 0.266 \text{ mA}$
 $V_i \geq 0.266 \times 10^{-3} \times 450 + 0.7 = 0.82 \text{ V}$

(c) $1.058 - 0.82 = 0.238 \text{ V}$

10.3

 

$$V_P = 0.7 + 0.7 + 0.7 = 2.1 \text{ V (Input diodes are off)}$$

$$I_B = (5 - 2.1)/5000 - 0.7/5000 = 0.58 - 0.14 = 0.44 \text{ mA}$$

$$I_{CS} = (5 - 0.2)/2000 = 2.4 \text{ mA}$$

The transistor is saturated because $I_B = 0.44 \text{ mA} \geq I_{CS}/h_{FE} = 2.4/20 \text{ mA} = 0.12 \text{ mA}$

10.4

(a) $I_R = (5 - 0.2)/2K = 2.4 \text{ mA}$

(b) $I_L = (5 - 0.9)/rK = 0.82 \text{ mA}$


(c) $I_{CS} = I_R + N I_L = 2.4 + 0.82N$

(d) $I_B h_{FE} = 0.44 \times 20 = 8.8 \text{ mA}$


$$I_{CS} = 2.4 + 0.82 N \leq I_B h_{FE} = 8.8$$

$$N \leq (8.8 - 2.4)/0.82 = 7.8$$

(e) Fanout = 7

 


10.5

 

- (a) $V_B(Q_1) = 2.1 \text{ V}$ $V_C(Q_1) = 1.4 \text{ V}$
 $V_B(Q_2) = 1.4 \text{ V}$ $V_C(Q_2) = 0.9 \text{ V}$
 $V_B(Q_3) = 0.7 \text{ V}$ $V_C(Q_3) = 0.2 \text{ V}$
 $V_E(Q_1) = 3.0 \text{ V}$ $V_E(Q_2) = 0.7 \text{ V}$
- (b) $I_{B1} = I_{B2} = (5 - 2.1)/4000 = 0.725 \text{ mA}$
 $I_{C2} = (5 - 0.9)/1600 = 2.56 \text{ mA}$
 $h_{FE}(Q2) \geq 2.56/0.726 = 3,53$
- (c) $I_{B3} = I_{B2} + I_{C2} - 0.7/1000 = 0.725 + 2.56 - 0.7 = 2.585 \text{ mA}$
- (d) $I_{C3} < I_{B3} \quad h_{FE} = 2.585 \times 6.18 = 16 \text{ mA}$
- (e) $(5 - 0.2)/R_L < 16 \text{ mA}$
- $R_L > 4.8 / 16 \times 10^{-3} = 4800/16 = 300$

10.6


- (a)**

 


If one or more transistor are ON, the output is at a low level. The output is high if and only if all transistors are off.

Q1	Q2	Output	AND
ON	ON	LOW	= 0
ON	OFF	LOW	= 0
OFF	ON	LOW	= 0
OFF	OFF	HIGH	= 1

(b) $A' B' = (A + B)'$

 

10.7

 

See Prob. 10.5

$$I_B(Q4) = (5 - 1.6)/1600 = 2.123 \text{ mA}$$

$$I_C(Q4) = (5 - 1.1)/130 = 30 \text{ mA}$$


$$I_L = I_B + I_C = 2.125 + 30 = 32.125 \text{ mA}$$

Note: 32 mA of current flows between the two circuits provided Q4 (of TTL -1) and Q3 (of TTL - 2) are both saturated.

10.8

	(a) C=L A=L	(b) C=L A=H	(c) C=L A=H
Q1 (base-emitter)	ON	OFF	ON
Q1(base-collector)	OFF	ON	OFF
Q2	OFF	ON	OFF
Q3 Totem-pole output	OFF	ON	OFF
Q4	ON	OFF	OFF
Q5	ON	OFF	OFF
Q6 (base-emittter)	ON	ON	OFF
Q6 (base-collector)	OFF	OFF	ON
Q7	OFF	OFF	ON
Q8	OFF	OFF	ON
State of output	HIGH	LOW	HIGH IMPEDANCE

 
- 10.9** (a) When one or more inputs are HIGH, Q5 is OFF and the input transistor(s) is ON.



$$I_E = (5.2 - 1.6)/779 = 4.62 \text{ mA}$$

$$V_{RC1} = 4.62 \times 10^{-3} \times 220 = 1.02 \text{ V}$$

 - (b) When all inputs are low, Q5 conducts and the input transistors are OFF.




$$I_E = (5.2 - 2.1)/779 = 4 \text{ mA}$$

$$V_{RC2} = 4 \times 10^{-3} \times 245 = 0.98 \text{ V}$$

- 10.10** Noise margin = $0.6 - 0.3 = 0.3 \text{ V}$


10.11

 

A	B	Y	OR
-1 V	-1 V	-1.8 V (L)	= 0
-1 V	GND	-0.8 V (H)	= 1
GND	-1 V	-0.8 V (H)	= 1
GND	GND	-0.8 V (H)	= 1


$$-1 \text{ V} = 0, \text{ GND} = 1$$

10.12

 


10.13


(a)

 

(b)

 


10.14

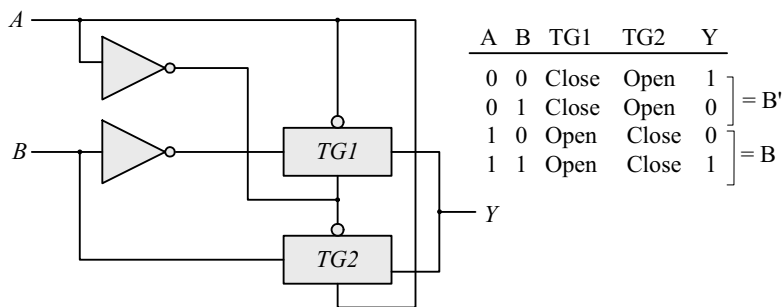

10.15

Add another level to the diagram of Fig. 10.26 and a third selection input, S_2 . The first level is controlled by S_0 and has 8 transmission gates between the data inputs and the four lines labeled $I_0 \dots I_3$ in Fig. 10.26. The other two levels are as in Fig. 10.26 except that the second level is controlled by S_1 and the third level is controlled by S_2 .

10.16

 

10.17

// Test bench for NAND2

```
module t_NAND2;
  reg A, B;
  wire Y;
```

```
  NAND2 M0 (Y, A, B);    // Instantiate NAND2
```

```
  initial #100 $finish;
```

```
  initial fork
```

```
    A = 0;
```

```
    B = 0;
```

```
    #5 B = 1;
```

```
    #10 A = 1;
```

```
    #15 B = 0;
```

```
  join
```

```
  initial $monitor ($time, "A = %b B = %b Y = %b", A, B, Y);
endmodule
```

//CMOS 2-input NAND Fig. 10.22(b)

```
module NAND2 (Y, A, B);
```

```
  input A, B;
```

```
  output Y;
```

```
  supply1 PWR;
```

```
  supply0 GRD;
```

```
  wire W1;    // terminal between two nmos
```

```
  pmos (Y, PWR, A); // source connected to Vdd
```

```
  pmos (Y, PWR, B); // parallel connection
```

```
  nmos (Y, W1, A);  // serial connection
```

```
  nmos (W1, GRD, B); // source connected to ground
```


```
endmodule
```

```
0 A = 0 B = 0 Y = 1
```

```
5 A = 0 B = 1 Y = 1
```

```
10 A = 1 B = 1 Y = 0
```


```
15 A = 1 B = 0 Y = 1
```

 

11.2 Truth table:



Inputs							
A	B	NAND	NOR	NOT(A)	AND	OR	XOR
0	0	1	0	1	0	0	0
0	1	1	1	0	0	1	1
1	0	1	1	1	0	1	1
1	1	0	1	0	1	1	0

Waveforms:

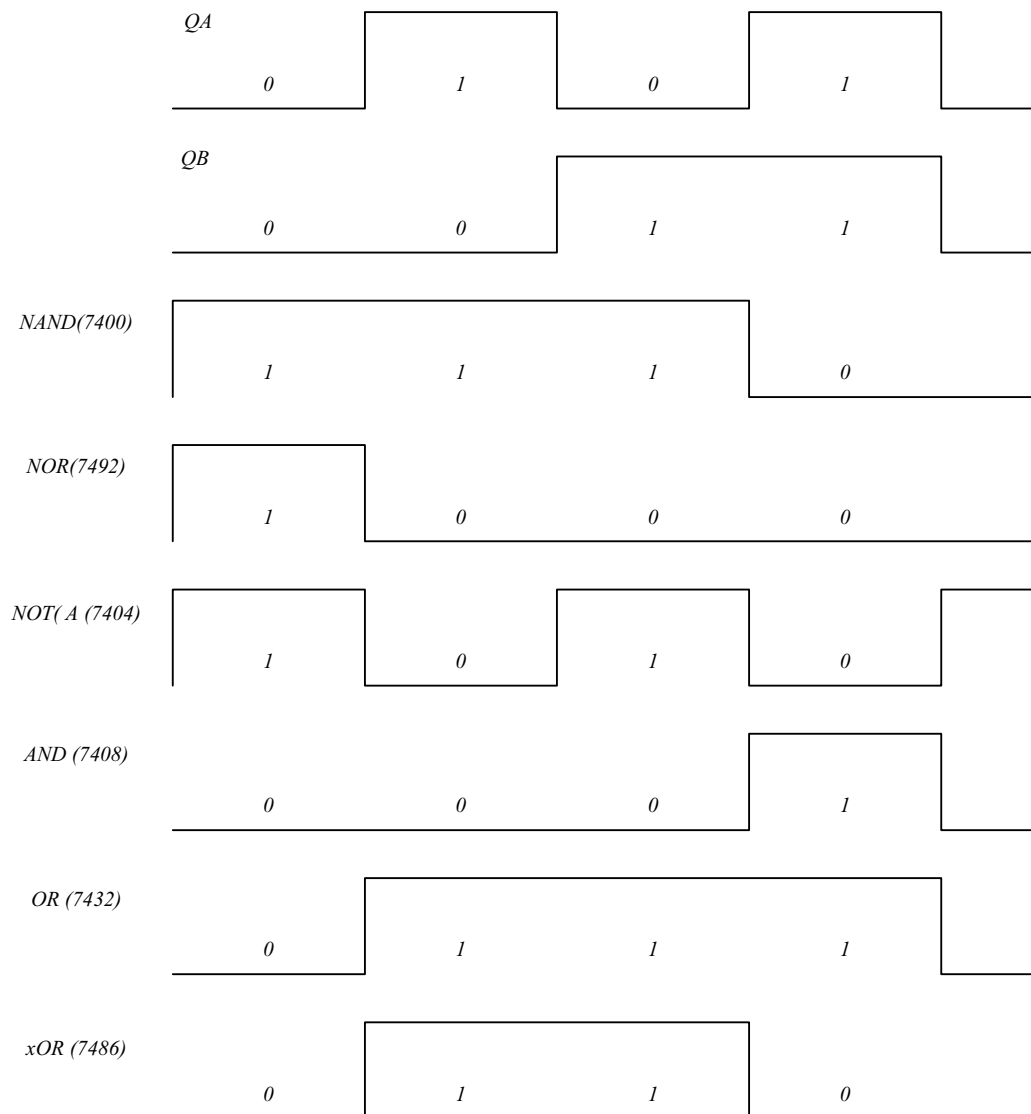


11.3

Logic Diagram

  


Boolean Functions:

 


$$F_1 = C' + AB'D'$$

Boolean Functions:

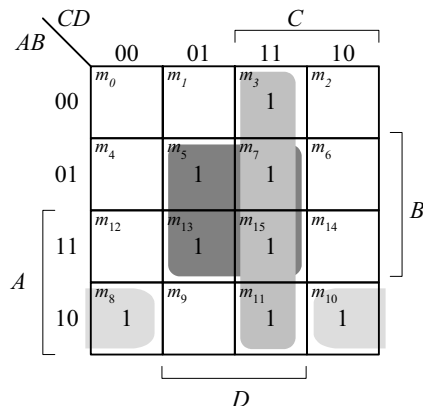

$$F_2 = BD + CD + AB'D'$$

2 ICs: 7400, 7410

 


Complement:

CD		C			
		00	01	11	10
AB	00	m_0 0	m_1 1	m_3 1	m_2 1
	01	m_4 0	m_5 1	m_7 1	m_6 0
	11	m_{12} 0	m_{13} 1	m_{15} 1	m_{14} 0
	10	m_8 0	m_9 1	m_{11} 1	m_{10} 1

$$F = D + B'C$$

$$F' = C'D' + BD'$$

 


2 - 7400 ICs

11.4

Design Example:

CD		C			
		00	01	11	10
AB	00	m_0	m_1	m_3	m_2
	01	m_4	m_5 1	m_7 1	m_6 1
	11	m_{12}	m_{13} 1	m_{15} 1	m_{14} 1
	10	m_8 1	m_9 1	m_{11} 1	m_{10} 1



$$F = AB' + BC + BD$$

 

Majority Logic

yz		y			
		00	01	11	10
x	0	m_0	m_1	m_3 1	m_2
	1	m_4	m_5 1	m_7 1	m_6 1

$$F = xy + xz + yz$$

  


Decoder Implementation

$$F_1 = xz + x'y'z' = \Sigma(0, 5, 7)$$

$$F_2 = x'y + xy'z' = \Sigma(2, 3, 4)$$

$$F_3 = xy + x'y'z = \Sigma(1, 6, 7)$$

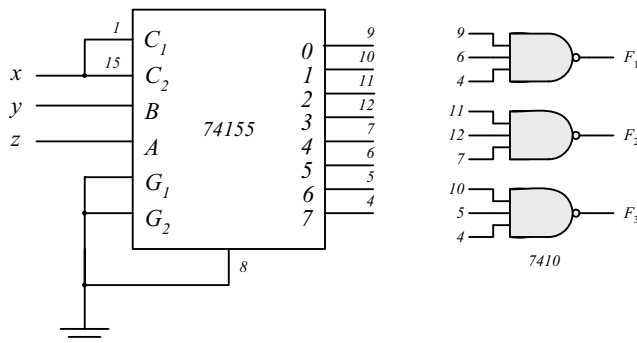

11.5 Gray code to Binary – See solution to Prob. 4.7.

9's complementer – See solution to Prob. 4.18.

$$w = A'B'C'$$


$$x = BC' + B'C$$

$$y = C$$


$$z = D'$$

$$E = AB + AC$$

3 ICs: 7400, 7404, 7410

 

11.6

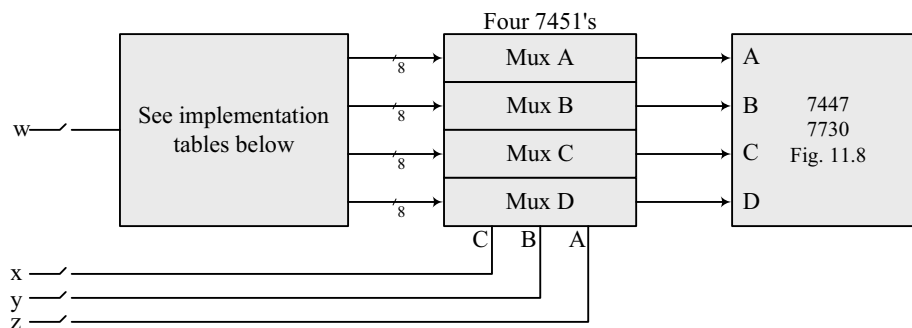


$$A = \sum(0, 2, 3, 6, 7, 8, 9, 12, 13)$$


$$B = \sum(0, 2, 3, 4, 5, 12, 13, 14)$$

$$C = \sum(0, 1, 3, 5, 6, 9, 10, 13, 14)$$

$$D = \sum(0, 7, 11)$$

 


11.7

 

Parallel adder - See circuit of Fig. 11.10.

Adder-subtractor - See circuit of Fig. 11.11.


Operation	Inputs				Outputs		
	M	A	B	C ₀	S	C ₄	
9 + 5 = 14	0	1001	0101	0	1110	0	
9 + 9 = 19 = 16 + 2	0	1001	1001	0	0010	1	sum < 15
9 + 15 = 24 = 16 + 8	0	1001	1111	0	1000	1	sum > 15
9 - 5 = 4	1	1001	0101	1	0100	1	sum > 15
9 - 9 = 0	1	1001	1001	1	0000	1	A > B
9 - 15 = -6	1	1001	1111	1	1010	0	A = B
							A < B

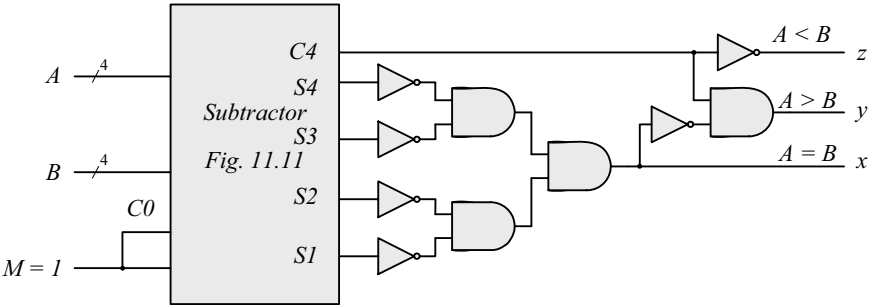

 11.8 **SR Latch:** See Fig. 5.4.


D Latch:

Let $CP = C$, x = output of gate 4.
 $x = [(DC)'C]' = (D'C)'$




Master-Slave D Flip-Flop: The circuit is as in Fig. 5.9.

The oscilloscope display:

 

 
Edge-Triggered D Flip-Flop: Circuit is shown in Fig. 5.10.



IC Flip-Flops:

Connect all inputs to toggle switches, the clock to a pulser, and the outputs to indicator lamps.

11.9 Up-Down Counter with Enable:

 

$$J_B = K_B = E \text{ (Complement B when } E = 1\text{)}$$

$$J_A = K_A = E (Bx + B'x')$$


Complement A when $E = 1$ and:

$B = 1$ when $x = 1$ (Count up)

$B = 0$ when $x = 0$ (Count down)

State Diagram:
 
$$\begin{aligned} J_A &= B & J_B &= Ax + A'x' = (A \oplus x)' & Y &= A \oplus B \oplus x \\ K_A &= B' & K_B &= Ax + A'x' = (A \oplus x)' \end{aligned}$$



Design of Counter: ABCD

$$\begin{aligned} J_A &= K_A = B(CD) & 0000 &\rightarrow 0101 \rightarrow 0110 \\ J_B &= K_B = CD & 1000 &\rightarrow 1001 \rightarrow 1010 \\ J_C &= D & K_C &= AD \\ J_D &= K_D = 1 \end{aligned}$$


11.10 Ripple counter: See Fig. 6.8

Down counter: Either take outputs from Q' outputs or connect complement Q' to next clock input.

Synchronous counter: See Fig. 6.12.

BCD counter: See solution to Prob. 6.19.

Unused states:

 

Binary counter with parallel load:

Connect QA and QD through a NAND gate to the load. See Fig. 6.15.

11.11 Ring counter:

See Fig. 6.17(a).

States of register:

QA	QB	QC	QD
1	0	0	0
0	1	0	0
0	0	1	0
0	0	0	1

Switch-tail ring counter: See Fig. 6.18(a). Connect (QD)' at pin 12 to the serial input at pin 4. State sequence as in Fig. 6.18(b).

Feedback shift register: Serial input = $QC \oplus QD$ (Use 7486).

Sequence of states:

QA	QB	QC	QD
1	0	0	0
0	1	0	0
0	0	1	0
1	0	0	1
1	1	0	0


Bidirectional shift register with parallel load:

Function table:


74195			74157		Function
Clear	Clock	SH/LD	STROBE	SELECT	
0	x	x	x	x	Async clear
1	↑	1	x	x	Shift right ($QA \rightarrow QB$)
1	↑	0	0	1	Shift left (Select B)*
1	↑	0	0	0	Parallel Load (Select A)
1	↑	0	1	x	Synchronous clear

* B inputs come from QA-QD shifted by one position.


11.12

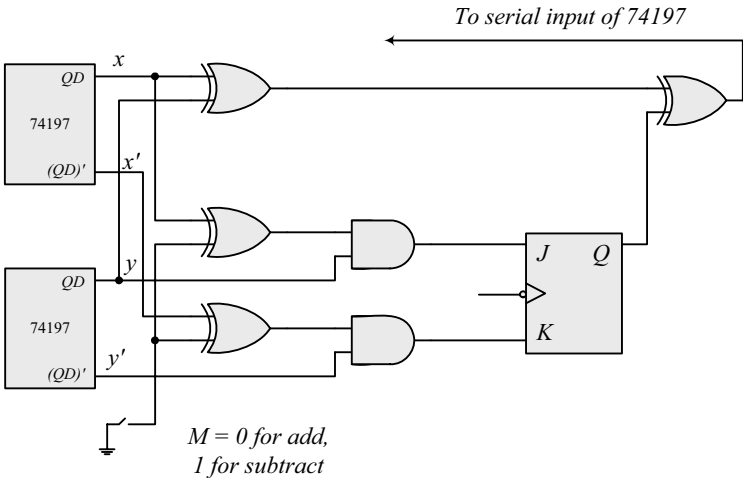

11.13 Testing the RAM:

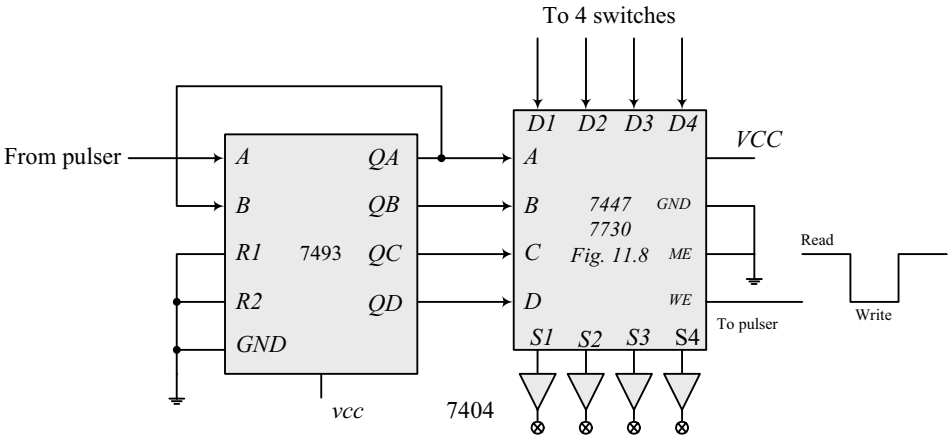

Memory Expansion:

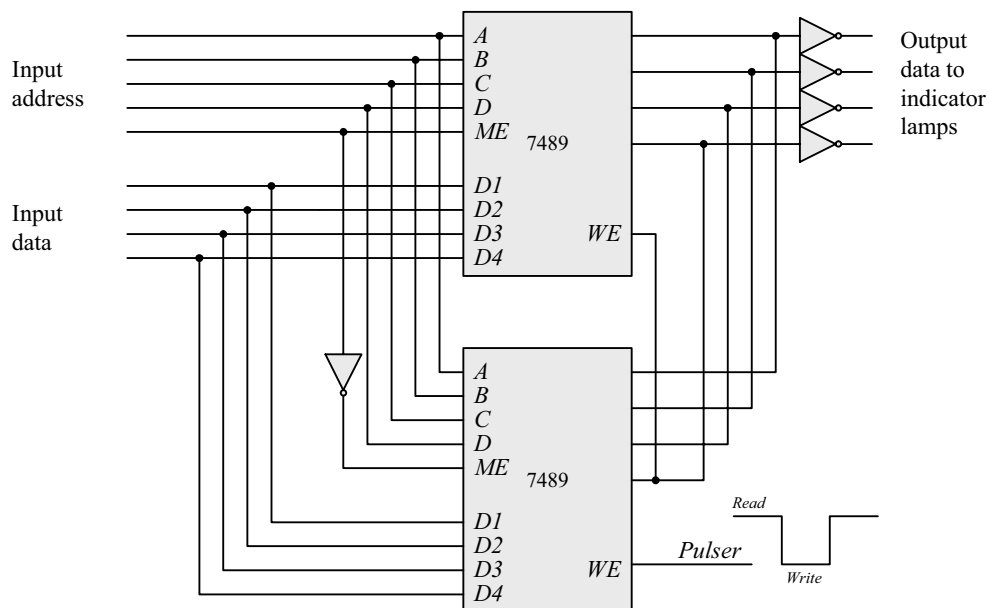

11.14 Circuit Analysis – Answers to questions:


- 1) Resets to 0 the two 74194 ICs, the two D flip-flops, and the start SR latch. This makes $SIS0 = 11$ (parallel load).
- 2) The start switch sets the SR latch to 1. The clock pulses load 0000_0001 into the 8-bit register. If the start switch stays on, the register never clears to all 0s when $SIS0 = 11$ (right-most QD stays on).
- 3) Pressing the pulser makes $SIS0 = 10$ and the light shifts left. When QC becomes 1, the start SR latch is cleared to 0. When QA of the left 74194 becomes 1, it changes $S1$ to 0 (through the PR input) and $S0$ to 1 (through the CLR input. with $SIS0 = 01$, the single light shifts right).
- 4) If the pulser is pressed while the light is moving to the left or the right, $SIS0$ becomes 11 and all 0s are loaded into the register in parallel. The light goes off.
- 5) When the right-most QD becomes a 1, $SIS0$ changes from 01 (shift right) to 11 (parallel load). If the pulser is pressed before the next clock pulse, $SIS0$ goes to 10 (shift left). If not pressed, an all 0s value is loaded into the register in parallel. (Provided the start switch is in the logic 1 position.)

Lamp Ping-Pong

Add a left pulser. Three wire changes to the D flip-flop on the left:

- 1) Connect the clock input of the flip-flop to the pulser.
- 2) Connect the D input to the QA of the left 74197
- 3) Connect the input of the inverter (that goes to PR) to ground.


Counting the Losses

 

 11.15 Clock Pulse Generator

$t_L = 0.693 R_B C = 10^{-6}$
 $R_B = 10^{-6} / (0.693 \times 0.001 \times 10^{-6}) = 10^3 / 0.693 = 1.44 \text{ K}\Omega$ (Use $R_B = 1.5 \text{ K}\Omega$)
 $t_H/t_L = 0.693 (R_A + R_B)C / (0.693 R_B C) = (R_A + R_B) / R_B = 9 / 1 = 9$
 $9 R_B = R_A + R_B \quad R_A = 8 R_B = 8 \times 1.5 \text{ K}\Omega = 12 \text{ K}\Omega$


Oscilloscope Waveforms (Actual results may be off by $\pm 20 \%$.)



Variable Frequency Pulse Generator:

20 KHz: $10^{-3} / 20 = 0.05 \times 10^{-3} = 50 \mu s$
100 KHz: $10^{-3} / 100 = 10^{-5} = 10 \mu s$
 $t_H = 49 \mu s: (R_A + R_P + R_B) / R_B = 49 / 1 = 49$
 $R_P = 48 R_B - R_A = 48 \times 1.5 - 11 = 60 \text{ K}\Omega$

11.15 Control of Register

 

Checking the Circuit:

	Carry	Register
Initial	0	0 0 0 0
+ 0110	0	0110
+ 1110	1	0100
+ 1101	1	0001
+ 0101	0	0110
+ 0011	0	1001

Circuit Operation:

Address	Carry	RAM	
0	0	0110	RAM Value
1	0	0110	RAM + Register
2	0	0011	Shift Register
3		1110	RAM Value
4	1	0001	RAM + Register
5	1	1000	SHIFT
6		1101	RAM Value
7	1	0101	RAM + Register
8	1	1010	SHIFT
9		0101	RAM Value
10	0	1111	RAM + Register
11	0	0111	SHIFT
12		0011	RAM Value
13	0	1010	RAM + Register
14	0	0101	SHIFT


11.17 Multiplication Example)11 x 15 = 165)

Multiplicand B = 1111

		C	A	Q	P
Initial:	T ₁ = 1	0	0000	1011	0000
T ₂ = 1	Add B; P <= P+1		1111		
		0	1111	1011	0001
T ₃ = 1	Shift CAQ	0	0111	1101	0001
T ₂ = 1	Add B; P <= P+1		1111		
		1	0110	1101	0010
T ₃ = 1	Shift CAQ	0	1011	0110	0010
T ₂ = 1	P <= P+1	0	1011	0110	0011
T ₃ = 1	Shift CAQ	0	0101	1011	0011
T ₂ = 1	Add B; P <= P+1		1111		
		1	0100	1011	0100
T ₃ = 1	Shift CAQ	0	1010	0101	0100
T ₀ = 1	(Because P _C = 1)		1010	0101	= Product

Load Q T ₁	Load A T ₂ Q ₁	Shift AQ T ₃	Register Q S ₁ S ₀	Register A S ₁ S ₀
0	0	0	0 0	0 0
1	0	0	1 1	0 0
0	1	0	0 0	1 1
0	0	1	0 1	0 1

 
$$\begin{aligned} S_1(A) &= T_2 Q_1 \\ S_0(A) &= T_2 Q_1 + T_3 \end{aligned}$$



SOLUTIONS FOR SECTION 11.20

Supplement to Experiment 2:

(a)

 

Initially, with $xy = 00$, $w1 = w2 = 1$, $w3 = w4 = 0$ and $F = 0$. $w1$ should change to 0 10ns after xy changes to 01. $w4$ should change to 1 20 ns after xy changes to 01. F should change from 0 to 1 30 ns after $w4$ changes from 0 to 1, i.e., 50 ns after xy changes from 00 to 01. $w3$ should remain unchanged because $x = 0$ for the entire simulation.

(b)

```
`timescale 1ns/1ps
```

```
module Prob_3_33 (output F, input x, y);
  wire w1, w2, w3, w4;
```

```
  and #20 (w3, x, w1);
  not #10 (w1, x);
  and #20 (w4, y, w2);
  not #10 (w2, y);
  or #30 (F, w3, w4);
```

```
endmodule
```

```
module t_Prob_3_33 ();
  reg x, y;
  wire F;
```

```
  Prob_3_33 M0 (F, x, y);
```

```
  initial #200 $finish;
```

```
  initial fork
```

```
    x = 0;
```


```
    y = 0;
```

```
    #100 y = 1;
```

```
  join
```

```
endmodule
```

 (c) To simulate the circuit, it is assumed that the inputs $xy = 00$ have been applied sufficiently long for the circuit to be stable before $xy = 01$ is applied. The testbench sets $xy = 00$ at $t = 0$ ns, and $xy = 1$ at $t = 100$ ns. The simulator assumes that $xy = 00$ has been applied long enough for the circuit to be in a stable state at $t = 0$ ns, and shows $F = 0$ as the value of the output at $t = 0$. The waveforms show the response to $xy = 01$ applied at $t = 100$ ns.



Supplement to Experiment 4:

(a)

// Gate-level description of circuit in Fig. 4-2

module Circuit_of_Fig_4_2 (

output F1, F2,

input A, B, C);

wire T1, T2, T3, F2_not, E1, E2, E3;

orG1 (T1, A, B, C);

and G2 (T2, A, B, C);

and G3 (E1, A, B);

and G4 (E2, A, C);

and G5 (E3, B, C);

orG6 (F2, E1, E2, E3);

not G7 (F2_not, F2);

and G8 (T3, T1, F2_not);

orG9 (F1, T2, T3);

endmodule

module t_Circuit_of_Fig_4_2;

reg [2: 0] D;

wire F1, F2;

parameter stop_time = 100;

Circuit_of_Fig_4_2 M1 (F1, F2, D[2], D[1], D[0]);

initial # stop_time \$finish;

initial begin // Stimulus generator

 D = 3'b000;

repeat (7)

 #10 D = D + 1'b1;

end

initial begin

\$display ("A B C F1 F2");


\$monitor ("%b %b %b %b %b", D[2], D[1], D[0], F1, F2);

end

endmodule

```
/*
A   B   C   F1  F2
0   0   0   0   0
0   0   1   1   0
0   1   0   1   0
0   1   1   0   1
1   0   0   1   0
1   0   1   0   1
1   1   0   0   1
1   1   1   1   1
*/
```

 The simulation results demonstrate the behavior of a full adder, with F1 = sum, and F2 – carry.



(b)

```
// 3-INPUT MAJORITY DETECTOR CIRCUIT.
// Circuit implements  $F = xy + xz + yz$ .
module Majority_Detector (output F, input x, y, z);
    wire w1, w2, w3;
    nand n1(w1, x, y),
        n2(w2, x, z),
        n3(w3, y, z),
        n4(F, w1, w2, w3);
endmodule

// Test bench
//Treating inputs to majority detector as a vector, reg [2:0]D; //D[2] = x, D[1] = y, D[0] = z. wire F;
module t_Majority_Detector ();
    wire F;
    reg [2: 0] D;
    wire x = D[2];
    wire y = D[1];
    wire z = D[0];

    Majority_Detector M0 (F, x, y, z);

    initial #100 $finish;
    initial $monitor ($time,, "xyz = %b F = %b", D, F);
```

initial begin

D = 0;

repeat (7)

#10 D = D + 1;

end

endmodule

Simulation results:

0 xyz = 000 F = 0

10 xyz = 001 F = 0

20 xyz = 010 F = 0


30 xyz = 011 F = 1

40 xyz = 100 F = 0

50 xyz = 101 F = 1

60 xyz = 110 F = 1

70 xyz = 111 F = 1

 

Supplement to Experiment 5: See the solution to Prob. 4.42.

Supplement to Experiment 7:

(a)

//BEHAVIORAL DESCRIPTION OF 7483 4-BIT ADDER,

module Adder_7483 (

output S4, S3, S2, S1, C4,

input A4, A3, A2, A1, B4, B3, B2, B1, C0, VCC, GND

);

// Note: connect VCC and GND to supply1 and supply0 in the test bench

wire [4: 1] sum;

wire [4: 1] A = {A4, A3, A2, A1};

wire [4: 1] B = {B4, B3, B2, B1};

assign S4 = sum[4];

assign S3 = sum[3];

assign S2 = sum[2];

assign S1 = sum[1];

assign {C4, sum} = A + B + C0;

endmodule

```

module t_Adder_7483 ();
  wire S4, S3, S2, S1, C4;
  wire A4, A3, A2, A1, B4, B3, B2, B1;
  reg C0;
  supply1 VCC;
  supply0 GND;
  reg [4:1] A, B;
  assign A4 = A[4];
  assign A3 = A[3];
  assign A2 = A[2];
  assign A1 = A[1];
  assign B4 = B[4];
  assign B3 = B[3];
  assign B2 = B[2];
  assign B1 = B[1];

  Adder_7483 M0 (S4, S3, S2, S1, C4, A4, A3, A2, A1, B4, B3, B2, B1, C0, VCC, GND);

  initial #2600 $finish;
  initial begin
    A = 0; B = 0; C0 = 0;
    repeat (256) #5 {A, B} = {A, B} + 1;
    A = 0; B = 0; C0 = 1;
    repeat (256) #5 {A, B} = {A, B} + 1;
  end
endmodule

```

(b)

```

module Supp_11_17b (output [4: 1] S, output carry, input [4: 1] A, B, input M, VCC, GND);
  wire B4, B3, B2, B1;
  xor (B4, M, B[4]);
  xor (B3, M, B[3]);
  xor (B2, M, B[2]);
  xor (B1, M, B[1]);
  Adder_7483 M0 (S[4], S[3], S[2], S[1], carry, A[4], A[3], A[2], A[1], B4, B3, B2, B1, M, VCC, GND);
endmodule

module Adder_7483 (
  output S4, S3, S2, S1, C4,
  input A4, A3, A2, A1, B4, B3, B2, B1, C0, VCC, GND
);
// Note: connect VCC and GND to supply1 and supply0 in the test bench
wire [4: 1] sum;
wire [4: 1] A = {A4, A3, A2, A1};
wire [4: 1] B = {B4, B3, B2, B1};
assign S4 = sum[4];
assign S3 = sum[3];
assign S2 = sum[2];
assign S1 = sum[1];
assign {C4, sum} = A + B + C0;
endmodule

```

```

module t_Supp_11_17b ();
  wire [4: 1] S;
  wire carry;
  reg C0;
  reg [4: 1] A, B;
  reg M;
  supply1 VCC;
  supply0 GND;

  Supp_11_17b M0 (S, carry, A, B, M, VCC, GND);
  initial #2600 $finish;
  initial begin
    A = 0; B = 0; M = 0;
    repeat (256) #5 {A, B} = {A, B} + 1;
    A = 0; B = 0; M = 1;
    repeat (256) #5 {A, B} = {A, B} + 1;
  end
endmodule

```

(c), (d)

```

module supp_11_7c (output S3, S2, S1, S0, C, V, input A3, A2, A1, A0, B3, B2, B1, B0, M);
  wire [3: 0] Sum, B;
  assign S3 = Sum[3];
  assign S2 = Sum[2];
  assign S1 = Sum[1];
  assign S0 = Sum[0];
  wire [3:0] A = {A3, A2, A1, A0};
  xor(B[3], B3, M);
  xor(B[2], B2, M);
  xor(B[1], B1, M);
  xor(B[0], B0, M);
  xor (V, C, C3);
  ripple_carry_4_bit_adder M0 (Sum, C, C3, A, B, M);
endmodule

```

```

module t_supp_11_7c ();
  wire S3, S2, S1, S0, C, V;
  reg A3, A2, A1, A0, B3, B2, B1, B0, M;
  wire [3: 0] sum = {S3, S2, S1, S0};
  wire [3: 0] A = {A3, A2, A1, A0};
  wire [3: 0] B = {B3, B2, B1, B0};

  supp_11_7c M0 (S3, S2, S1, S0, C, V, A3, A2, A1, A0, B3, B2, B1, B0, M);

  initial #2600 $finish;
  initial begin
    {A3, A2, A1, A0, B3, B2, B1, B0} = 0; M = 0;
    repeat (256) #5 {A3, A2, A1, A0, B3, B2, B1, B0} = {A3, A2, A1, A0, B3, B2, B1, B0} + 1;
    {A3, A2, A1, A0, B3, B2, B1, B0} = 0; M = 1;
    repeat (256) #5 {A3, A2, A1, A0, B3, B2, B1, B0} = {A3, A2, A1, A0, B3, B2, B1, B0} + 1;
  end
endmodule

```

```

module half_adder (output S, C, input x, y);    // Verilog 2001, 2005 syntax
// Instantiate primitive gates
  xor (S, x, y);
  and (C, x, y);
endmodule

module full_adder (output S, C, input x, y, z);
  wire S1, C1, C2;


// Instantiate half adders
  half_adder HA1 (S1, C1, x, y);
  half_adder HA2 (S, C2, S1, z);
  or G1 (C, C2, C1);
endmodule

// Modify for C3 output
module ripple_carry_4_bit_adder ( output [3: 0] Sum, output C4, C3, input [3:0] A, B, input C0);
  wire C1, C2; // Intermediate carries
// Instantiate chain of full adders
  full_adder FA0 (Sum[0], C1, A[0], B[0], C0),
              FA1 (Sum[1], C2, A[1], B[1], C1),
              FA2 (Sum[2], C3, A[2], B[2], C2),
              FA3 (Sum[3], C4, A[3], B[3], C3);


endmodule

```

Addition:

 

Subtraction:

 

Supplement to Experiment 8:

(a)

```
module Flip_flop_7474 (output reg Q, input D, CLK, preset, clear);
    always @ (posedge CLK, negedge preset, negedge clear)
    if (!preset)      Q <= 1'b1;
    else if (!clear)  Q <= 1'b0;
    else              Q <= D;
endmodule
```


```
module t_Flip_flop_7474 ();
    wire Q;
    reg D, CLK, preset, clear;
```

```
Flip_flop_7474 M0 (Q, D, CLK, preset, clear);
```

```
initial #150 $finish;
initial begin CLK = 0; forever #5 CLK = ~CLK; end
```

```
initial fork
    preset = 0; clear = 0;
    #20 preset = 1;
    #40 clear = 1;
join
```
 
```
initial begin D = 0; #60 forever #20 D = ~D; end
endmodule
```



(b)

//Solution to supplement Experiment 8(b)

//Behavioral description of a 7474 D flip-flop with Q_not

```
module Flip_Flop_7474_with_Q_not (output reg Q, Q_not, input D, CLK, Preset, Clear);
```

```
    always @ (posedge CLK, negedge Preset, negedge Clear)
```

```
    /* case ({Preset, Clear})
```

```
        2'b00: begin Q <= 1; Q_not <= 1; end
```

```
        2'b01: begin Q <= 1; Q_not <= 0; end
```

```
        2'b10: begin Q <= 0; Q_not <= 1; end
```

```
        2'b11: begin Q <= D; Q_not <= ~D; end
```

```
    // NOTE: Q_not <= ~Q will produce a pipeline effect and delay Q_not by one clock
```

```
    endcase*/
```

```
    if (Preset == 0) begin Q <= 1; if (Clear == 0) Q_not <= 1; else Q_not <= 0; end
```

```
    else if (Clear == 0) begin Q <= 0; Q_not <= 1; end
```



```
else begin Q <= D; Q_not <= ~D; end
endmodule
```

// Note: this model will not work if Preset and Clear are // both brought low and then high again.
// A case statement for both Q and Q_not is also OK.

```
module t_Flip_Flop_7474_with_Q_not ();
```

```
  wire Q, Q_not;
```

```
  reg D, CLK, Preset, Clear;
```

```
  Flip_Flop_7474_with_Q_not M0 (Q, Q_not, D, CLK, Preset, Clear);
```

```
  initial #250 $finish;
```


```
  initial begin CLK = 0; forever #5 CLK = ~CLK; end
```

```
  initial fork
```

```
    Preset = 1; Clear = 1;
```

```
    #50 Preset = 0;
```

```
    #80 Clear =
```

 

Supplement to Experiment #9:

(a)

```
module Figure_11_9a (output reg y, input x, clock, reset_b);
```

```
  reg [1: 0] state, next_state;
```

```
  parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;
```

```
  always @ (posedge clock, negedge reset_b) if (reset_b == 0) state <= S0; else state <= next_state;
```

```
  always @ (state, x) begin
```

```
    y = 0;
```

```
    case (state)
```

```
      S0:if (x) begin next_state = S0; y = 1; end else begin next_state = S1; y = 0; end
```

```
      S1:if (x) begin next_state = S3; y = 0; end else begin next_state = S2; y = 1; end
```

```
      S2:if (x) begin next_state = S1; y = 0; end else begin next_state = S0; y = 1; end
```

```
      S3:if (x) begin next_state = S2; y = 1; end else begin next_state = S3; y = 0; end
```

```
    endcase
```

```
  end
```

```
endmodule
```

```
module t_Figure_11_9a ();
```

```
  wire y;
```

```
  reg x, clock, reset_b;
```

```
  Figure_11_9a M0 (y, x, clock, reset_b);
```


```
  initial #200 $finish;
```

```
  initial begin clock = 0; forever #5 clock = ~clock; end
```

```

initial fork
  reset_b = 0;
  x = 0;      // S0. S1, S2 after release of reset_b
  #10 reset_b = 1;
  #40 x = 1;   // Stay in S0
  #60 x = 0;   // S1, S2
  #80 x = 1;   // s1, S3,
  #100 x = 0; // S3
  #130 x = 1;  // S2, S1, S3 cycle
join
endmodule

```

 

(b) The solution depends on the particular design.

(c, d)

Note: The HDL description of the state diagram produces outputs $T0$, $T1$, and $T2$. Additional logic must form the signals that control the datapath unit (*Load_regs*, *Incr_P*, *Add_regs*, and *Shift_regs*). An alternative controller that generates the control signals, rather than the states, as the outputs is given below too. It produces identical simulation results.

```

module Supp_11_9cd # (parameter dp_width = 5)
(
  output [2*dp_width - 1: 0] Product,
  output Ready,
  input [dp_width - 1: 0] Multiplicand, Multiplier,
  input Start, clock, reset_b
);
  wire Load_regs, Incr_P, Add_regs, Shift_regs, Done, Q0;

  Controller M0 (
    Ready, Load_regs, Incr_P, Add_regs, Shift_regs, Start, Done, Q0,
    clock, reset_b
  );

  Datapath M1(Product, Q0, Done, Multiplicand, Multiplier,
    Start, Load_regs, Incr_P, Add_regs, Shift_regs, clock, reset_b);
endmodule

```

/* // This alternative controller directly produces the signals needed to control the datapath.

```

module Controller (
  output Ready,
  output reg Load_regs, Incr_P, Add_regs, Shift_regs,
  input Start, Done, Q0, clock, reset_b
);

  parameter S_idle = 3'b001, // one-hot code
             S_add = 3'b010,
             S_shift = 3'b100;

```

```

reg [2: 0]    state, next_state;    // sized for one-hot
assign      Ready = (state == S_idle);

always @ (posedge clock, negedge reset_b)
    if (~reset_b) state <= S_idle; else state <= next_state;

always @ (state, Start, Q0, Done) begin
    next_state = S_idle;
    Load_regs = 0;
    Incr_P = 0;
    Add_regs = 0;
    Shift_regs = 0;
    case (state)
        S_idle: if (Start) begin next_state = S_add; Load_regs = 1; end
        S_add:  begin next_state = S_shift; Incr_P = 1; if (Q0) Add_regs = 1; end
        S_shift: begin Shift_regs = 1;
                    if (Done) next_state = S_idle;
                    else next_state = S_add;
                end
        default: next_state = S_idle;
    endcase
end
endmodule
*/

// This controller has an embedded unit to generate T0, T1, and T2 and additional logic to form // // the
signals needed to control the datapath.

module Controller (
    output Ready, Load_regs, Incr_P, Add_regs, Shift_regs,
    input Start, Done, Q0, clock, reset_b
);

    State_Generator M0 (T0, T1, T2, Start, Done, Q0, clock, reset_b);
    assign Ready = T0;
    assign Load_regs = T0 && Start;
    assign Incr_P = T1;
    assign Add_regs = T1 && Q0;
    assign Shift_regs = T2;
endmodule

module State_Generator (output T0,T1, T2, input Start, Done, Q0, clock, reset_b);
    parameter      S_idle = 3'b001,        // one-hot code
                  S_add  = 3'b010,
                  S_shift = 3'b100;

    reg [2: 0]    state, next_state;    // sized for one-hot
    assign  T0 = (state == S_idle);
    assign  T1 = (state == S_add);
    assign  T2 = (state == S_shift);

    always @ (posedge clock, negedge reset_b)
        if (~reset_b) state <= S_idle; else state <= next_state;

```

```

always @ (state, Start, Q0, Done) begin
    next_state = S_idle;
    case (state)
        S_idle:    if (Start) next_state = S_add;
        S_add:     next_state = S_shift;
        S_shift:   if (Done) next_state = S_idle; else next_state = S_add;
        default:   next_state = S_idle;
    endcase
end
endmodule

module Datapath #(parameter dp_width = 5, BC_size = 3) (
    output [2*dp_width - 1: 0] Product, output Q0, output Done,
    input [dp_width - 1: 0] Multiplicand, Multiplier,
    input Start, Load_regs, Incr_P, Add_regs, Shift_regs, clock, reset_b
);
// Default configuration: 5-bit datapath
reg [dp_width - 1: 0]    A, B, Q;           // Sized for datapath
reg                    C;
reg [BC_size - 1: 0]    P;                // Bit counter

assign Q0 = Q[0];
assign Done = (P == dp_width);           // Multiplier is exhausted
assign Product = {C, A, Q};
always @ (posedge clock, negedge reset_b)
    if (reset_b == 0) begin                // Added to this solution, but
        P <= 0;                            // not really necessary since Load_regs
        B <= 0;                            // initializes the datapath
        C <= 0;
        A <= 0;
        Q <= 0;
    end
    else begin
        if (Load_regs) begin
            P <= 0;
            A <= 0;
            C <= 0;
            B <= Multiplicand;
            Q <= Multiplier;
        end
        if (Add_regs) {C, A} <= A + B;
        if (Shift_regs) {C, A, Q} <= {C, A, Q} >> 1;
        if (Incr_P) P <= P+1 ;
    end
endmodule

module t_Supp_11_9cd;
    parameter dp_width = 5;                // Width of datapath
    wire [2 * dp_width - 1: 0] Product;
    wire Ready;
    reg [dp_width - 1: 0] Multiplicand, Multiplier;
    reg Start, clock, reset_b;
    integer Exp_Value;
    reg Error;

    Supp_11_9cd M0(Product, Ready, Multiplicand, Multiplier, Start, clock, reset_b);

    initial #115000 $finish;
    initial begin clock = 0; #5 forever #5 clock = ~clock; end

```


```

initial fork
    reset_b = 1;
    #2 reset_b = 0;
    #3 reset_b = 1;
join
always @ (negedge Start) begin
    Exp_Value = Multiplier * Multiplicand;
    //Exp_Value = Multiplier * Multiplicand + 1; // Inject error to confirm detection
end
always @ (posedge Ready) begin
    # 1 Error <= (Exp_Value ^ Product);
end

initial begin
    #5 Multiplicand = 0;
    Multiplier = 0;

    repeat (32) #10 begin
        Start = 1;
        #10 Start = 0;
        repeat (32) begin
            Start = 1;
            #10 Start = 0;
            #100 Multiplicand = Multiplicand + 1;
        end
        Multiplier = Multiplier + 1;
    end
end
endmodule

```

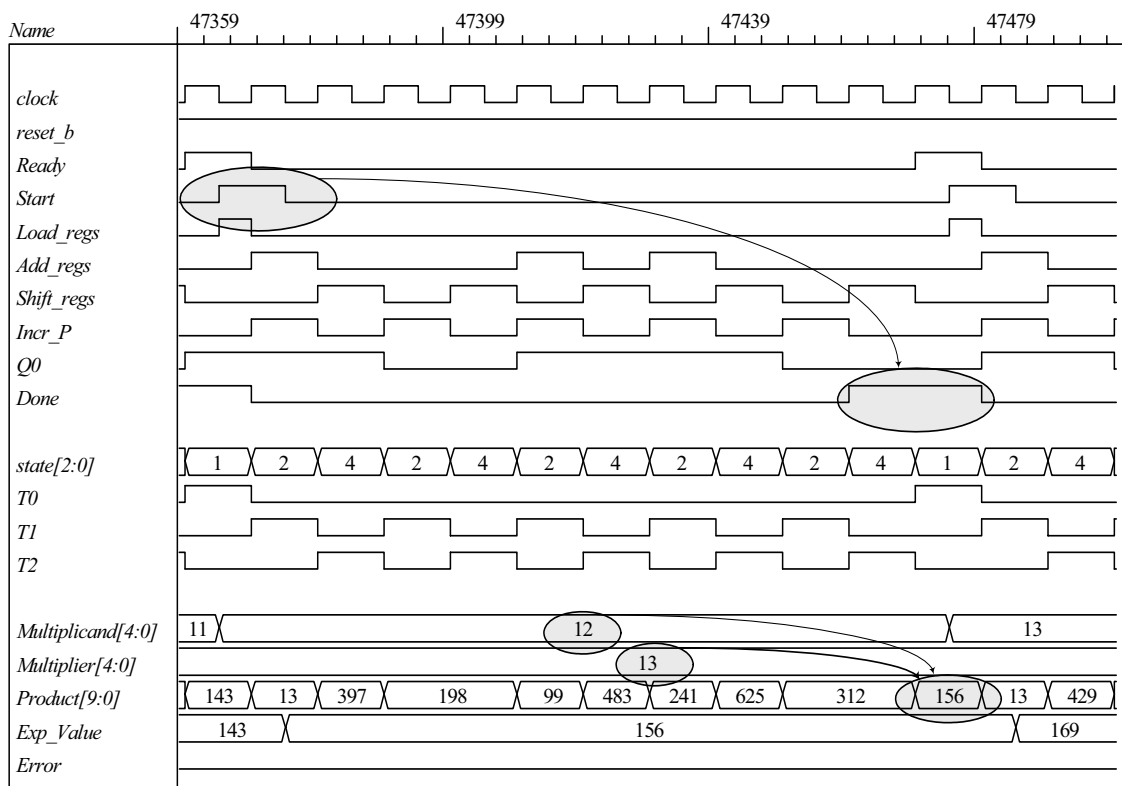

Supplement to Experiment #10:

```

module Counter_74161 (
    output      QD, QC, QB, QA,    // Data output
    output      COUT,             // Output carry
    input       D, C, B, A,       // Data input
    input       P, T,             // Active high to count
    L,          // Active low to load
    CK,         // Positive edge sensitive
    CLR         // Active low to clear
);

    reg [3: 0] A_count;
    assign QD = A_count[3];
    assign QC = A_count[2];
    assign QB = A_count[1];
    assign QA = A_count[0];

    assign COUT = ((P == 1) && (T == 1) && (L == 1) && (A_count == 4'b1111));

    always @ (posedge CK, negedge CLR)
    if (CLR == 0)      A_count <= 4'b0000;
    else if (L == 0)   A_count <= {D, C, B, A};
    else if ((P == 1) && (T == 1)) A_count <= A_count + 1'b1;
    else A_count <= A_count; // redundant statement
endmodule


module t_Counter_74161 ();
    wire      QD, QC, QB, QA;
    wire [3: 0] Data_outputs = {QD, QC, QB, QA};
    wire      Carry_out;    // Output carry
    reg [3:0] Data_inputs;  // Data input
    reg       Count,        // Active high to count
    Load,    // Active low to load
    Clock,    // Positive edge sensitive
    Clear;    // Active low to clear

    Counter_74161 M0 (QD, QC, QB, QA, Carry_out,
        Data_inputs[3], Data_inputs[2], Data_inputs[1], Data_inputs[0], Count, Count, Load, Clock, Clear);

    initial #200 $finish;
    initial begin Clock = 0; forever #5 Clock = ~Clock; end

    initial fork
        Clear = 0;
        Load = 1;
        Count = 0;
        #20 Clear = 1;
        #40 Load = 0;
        #50 Load = 1;
        #80 Count = 1;
        #180 Count = 0;
        Data_inputs = 4'ha;    // 10
    join
endmodule

```

 

Supplement to Experiment #11.

(a)

// Note: J and K_bar are assumed to be connected together.


```
module SReg_74195 (
    output reg QA, QB, QC, QD,
    output QD_bar,
    input A, B, C, D, SH_LD, J, K_bar, CLR_bar, CK
);
    assign QD_bar = ~QD;

    always @ (posedge CK, negedge CLR_bar)
        if (!CLR_bar) {QA, QB, QC, QD} <= 4'b0;
        else if (!SH_LD) {QA, QB, QC, QD} <= {A, B, C, D};
        else case ({J, K_bar})
            2'b00: {QA, QB, QC, QD} <= {1'b0, QA, QB, QC};
            2'b11: {QA, QB, QC, QD} <= {1'b1, QA, QB, QC};
            2'b01: {QA, QB, QC, QD} <= {QA, QA, QB, QC}; // unused
            2'b10: {QA, QB, QC, QD} <= {~QA, QA, QB, QC}; // unused
        endcase
endmodule
```

```
module t_SReg_74195 ();
    wire QA, QB, QC, QD;
    wire QD_bar;
    reg A, B, C, D, SH_LD, CLR_bar, CK;
    reg Serial_Input;
    wire J = Serial_Input;
    wire K_bar = Serial_Input;
    wire [3:0] Data_inputs = {A, B, C, D};
    wire [3:0] Data_outputs = {QA, QB, QC, QD};
```

SReg_74195 M0 (QA, QB, QC, QD, QD_bar, A, B, C, D, SH_LD, J, K_bar, CLR_bar, CK);
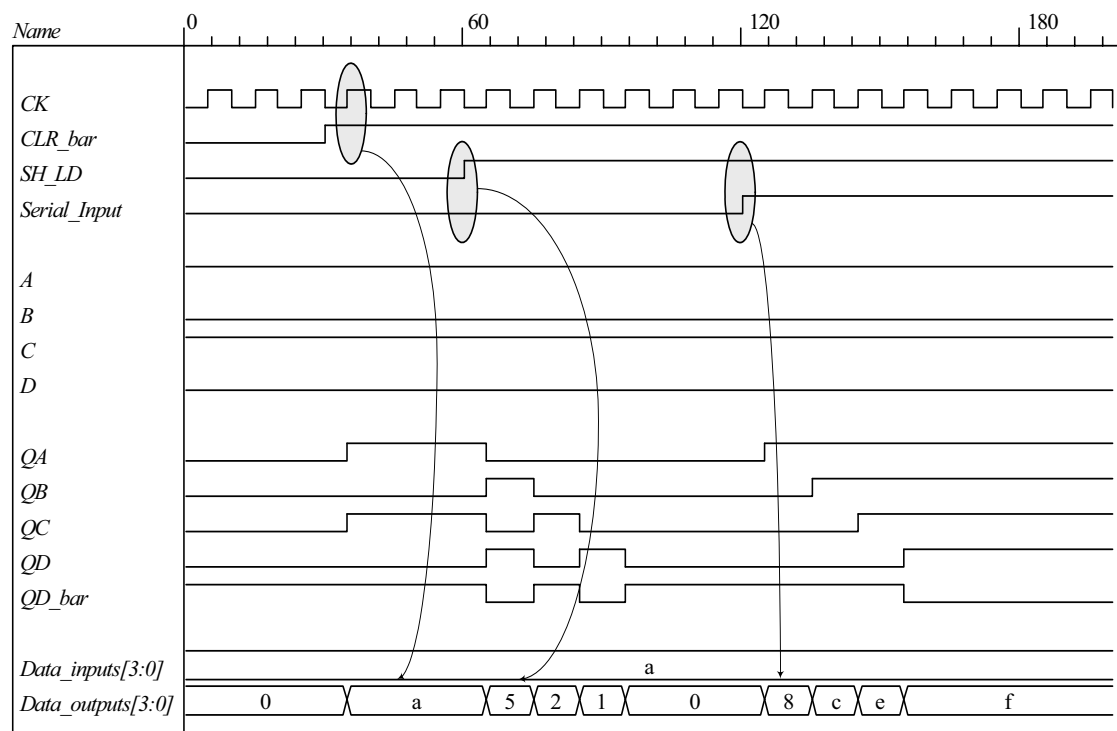
```
initial #200 $finish;
initial begin CK = 0; forever #5 CK = ~CK; end
initial fork
    {A, B, C, D} = 4'ha;
    CLR_bar = 0;
    Serial_Input = 0;
    SH_LD = 0;
    #30 CLR_bar = 1;
    #60 SH_LD = 1;
    #120 Serial_Input = 1;
join
endmodule
```



(b)


```
module Mux_74157 (
    output reg Y1, Y2, Y3, Y4,
    input A1, A2, A3, A4, B1, B2, B3, B4, SEL, STB
);
    wire [4: 1] In_A = {A1, A2, A3, A4};
    wire [4: 1] In_B = {B1, B2, B3, B4};
```

```
    always @ (In_A, In_B, SEL, STB)
        if (STB) {Y1, Y2, Y3, Y4} = 4'b0;
        else if (SEL) {Y1, Y2, Y3, Y4} = In_B;
        else {Y1, Y2, Y3, Y4} = In_A;
endmodule
```

```
module t_Mux_74157 ();
    wire Y1, Y2, Y3, Y4;
    reg A1, A2, A3, A4, B1, B2, B3, B4, SEL, STB;
    wire [4: 1] In_A = {A1, A2, A3, A4};
    wire [4: 1] In_B = {B1, B2, B3, B4};
    wire [4: 1] Y = {Y1, Y2, Y3, Y4};
```

Mux_74157 M0 (Y1, Y2, Y3, Y4, A1, A2, A3, A4, B1, B2, B3, B4, SEL, STB);
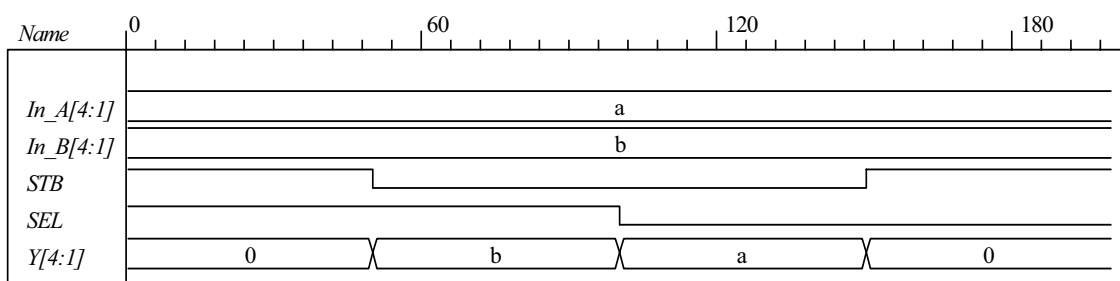
```
initial #200 $finish;
initial fork
    {A1, A2, A3, A4} = 4'ha;
    {B1, B2, B3, B4} = 4'hb;
    STB = 1;
    SEL = 1;
    #50 STB = 0;
    #100 SEL = 0;
    #150 STB = 1;
join
endmodule
```



(c)

```
module Bi_Dir_Shift_Reg (output [1: 4] D_out, input [1: 4] D_in, input SEL, STB, SH_LD, clock,
CLR_bar);
    wire QD_bar;
    wire [1: 4] Y;
    SReg_74195 M0 (D_out[1], D_out[2], D_out[3], D_out[4], QD_bar, Y[1], Y[2], Y[3], Y[4],
        SH_LD, D_out[4], D_out[4], CLR_bar, clock
    );
```


```
Mux_74157 M1 (Y[1], Y[2], Y[3], Y[4], D_in[1], D_in[2], D_in[3], D_in[4],
D_out[2], D_out[3], D_out[4], D_out[1], SEL, STB
);
endmodule
```

```
module SReg_74195 (
output reg QA, QB, QC, QD,
output QD_bar,
input A, B, C, D, SH_LD, J, K_bar, CLR_bar, CK
);
assign QD_bar = ~QD;
always @ (posedge CK, negedge CLR_bar)
if (!CLR_bar) {QA, QB, QC, QD} <= 4'b0;
else if (!SH_LD) {QA, QB, QC, QD} <= {A, B, C, D};
else case ({J, K_bar})
2'b00: {QA, QB, QC, QD} <= {1'b0, QA, QB, QC};
2'b11: {QA, QB, QC, QD} <= {1'b1, QA, QB, QC};
2'b01: {QA, QB, QC, QD} <= {QA, QA, QB, QC}; // unused
2'b10: {QA, QB, QC, QD} <= {~QA, QA, QB, QC}; // unused
endcase
endmodule
```


```
module Mux_74157 (
output reg Y1, Y2, Y3, Y4,
input A1, A2, A3, A4, B1, B2, B3, B4, SEL, STB
);
wire [4: 1] In_A = {A1, A2, A3, A4};
wire [4: 1] In_B = {B1, B2, B3, B4};

always @ (In_A, In_B, SEL, STB)
if (STB) {Y1, Y2, Y3, Y4} = 4'b0;
else if (SEL) {Y1, Y2, Y3, Y4} = In_B; // SEL = 1
else {Y1, Y2, Y3, Y4} = In_A; // SEL = 0
endmodule
```

```
module t_Bi_Dir_Shift_Reg ();
wire [1: 4] D_out;
reg [1: 4] D_in;
reg SEL, STB, SH_LD, clock, CLR_bar;
Bi_Dir_Shift_Reg M0 (D_out, D_in, SEL, STB, SH_LD, clock, CLR_bar);
initial #200 $finish;
initial begin clock = 0; forever #5 clock = ~clock; end
initial fork
D_in = 4'h8; // Data for walking 1 to right
CLR_bar = 0;
STB = 0;
SEL = 0; // Selects D_in
SH_LD = 0; // load D_in
#10 CLR_bar = 1;
#20 STB = 1;
#40 STB = 0;
#30 SH_LD = 1;
#50 SH_LD = 0; // Interrupt count to load
#60 SH_LD = 1;
#80 SEL = 1;
#100 STB = 1;
#130 STB = 0;
#140 SH_LD = 0;
// #150 SH_LD = 1;
join
endmodule
```

 

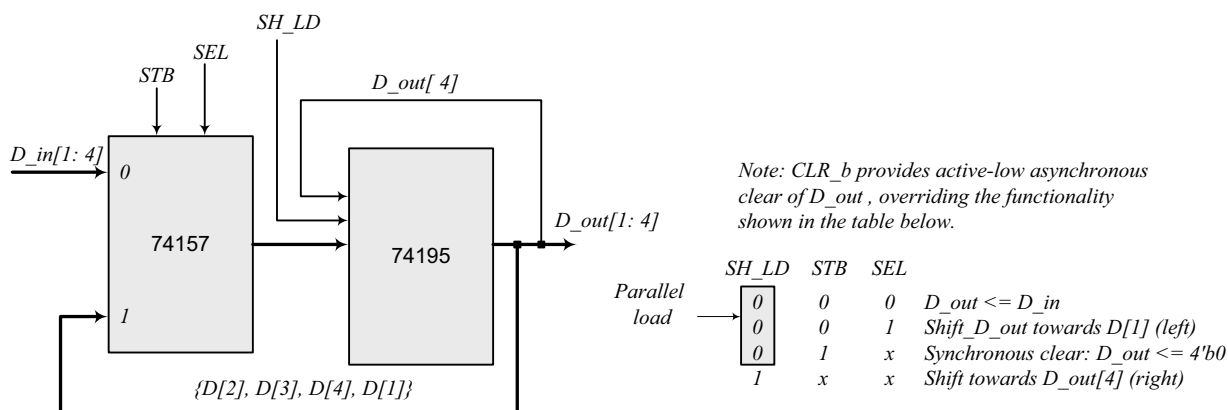The behavioral model is listed below. The two models have matching simulation results.



```

module Bi_Dir_Shift_Reg_beh (output reg [1: 4] D_out, input [1: 4] D_in, input SEL, STB, SH_LD, clock,
CLR_bar);
always @ (posedge clock, negedge CLR_bar)
    if (!CLR_bar) D_out <= 4'b0;
    else if (SH_LD) D_out <= {D_out[4], D_out[1], D_out[2], D_out[3]};
    else if (!STB) D_out <= SEL ? {D_out[2: 4], D_out[1]}: D_in;
    else D_out <= 4'b0;
endmodule

```

```

module t_Bi_Dir_Shift_Reg_beh ();
wire [1: 4] D_out;
reg [1: 4] D_in;
reg SEL, STB, SH_LD, clock, CLR_bar;

```

```

Bi_Dir_Shift_Reg_beh M0 (D_out, D_in, SEL, STB, SH_LD, clock, CLR_bar);

```

```

initial #200 $finish;

```

```

initial begin clock = 0; forever #5 clock = ~clock; end
initial fork
    D_in = 4'h8;          // Data for walking 1 to right
    CLR_bar = 0;
    STB = 0;
    SEL = 0;              // Selects D_in
    SH_LD = 0;           // load D_in
    #10 CLR_bar = 1;
    #20 STB = 1;
    #40 STB = 0;
    #30 SH_LD = 1;
    #50 SH_LD = 0;        // Interrupt count to load
    #60 SH_LD = 1;
    #80 SEL = 1;
    #100 STB = 1;
    #130 STB = 0;
    #140 SH_LD = 0;
    // #150 SH_LD = 1;
join
endmodule

```

Supplement to Experiment #13.

```

module RAM_74189 (output S4, S3, S2, S1, input D4, D3, D2, D1, A3, A2, A1, A0, CS, WE);
// Note: active-low CS and WE
wire [3: 0]          address = {A3, A2, A1, A0};
reg [3: 0]           RAM [0: 15];          // 16 x 4 memory
wire [4: 1]          Data_in = { D4, D3, D2, D1}; // Input word
tri [4: 1]           Data;                // Output data word, three-state output
assign S1 = Data[1];          // Output bits
assign S2 = Data[2];
assign S3 = Data[3];
assign S4 = Data[4];

always @ (Data_in, address, CS, WE) if (~CS && ~WE) RAM[address] = Data_in;
assign Data = (~CS && WE) ? ~RAM[address] : 4'bz;
endmodule

```

```

module t_RAM_74189 ();
reg [4: 1] Data_in;
reg [3: 0] address;
reg CS, WE;
wire S1, S2, S3, S4;
wire D1, D2, D3, D4;
wire A0, A1, A2, A3;
wire [4: 1] Data_out = {S4, S3, S2, S1};
assign D1 = Data_in [1];
assign D2 = Data_in [2];
assign D3 = Data_in [3];
assign D4 = Data_in [4];
assign A0 = address[0];
assign A1 = address[1];
assign A2 = address[2];
assign A3 = address[3];


wire [3: 0] RAM_0 = M0.RAM[0];
wire [3: 0] RAM_1 = M0.RAM[1];
wire [3: 0] RAM_2 = M0.RAM[2];
wire [3: 0] RAM_3 = M0.RAM[3];
wire [3: 0] RAM_4 = M0.RAM[4];

```

```
wire [3: 0] RAM_5 = M0.RAM[5];  
wire [3: 0] RAM_6 = M0.RAM[6];  
wire [3: 0] RAM_7 = M0.RAM[7];  
wire [3: 0] RAM_8 = M0.RAM[8];  
wire [3: 0] RAM_9 = M0.RAM[9];  
wire [3: 0] RAM_10 = M0.RAM[10];  
wire [3: 0] RAM_11 = M0.RAM[11];  
wire [3: 0] RAM_12= M0.RAM[12];  
wire [3: 0] RAM_13 = M0.RAM[13];  
wire [3: 0] RAM_14 = M0.RAM[14];  
wire [3: 0] RAM_15 = M0.RAM[15];  
wire [4: 1] word = ~Data_out;
```

```
RAM_74189 M0 (S4, S3, S2, S1, D4, D3, D2, D1, A3, A2, A1, A0, CS, WE);
```
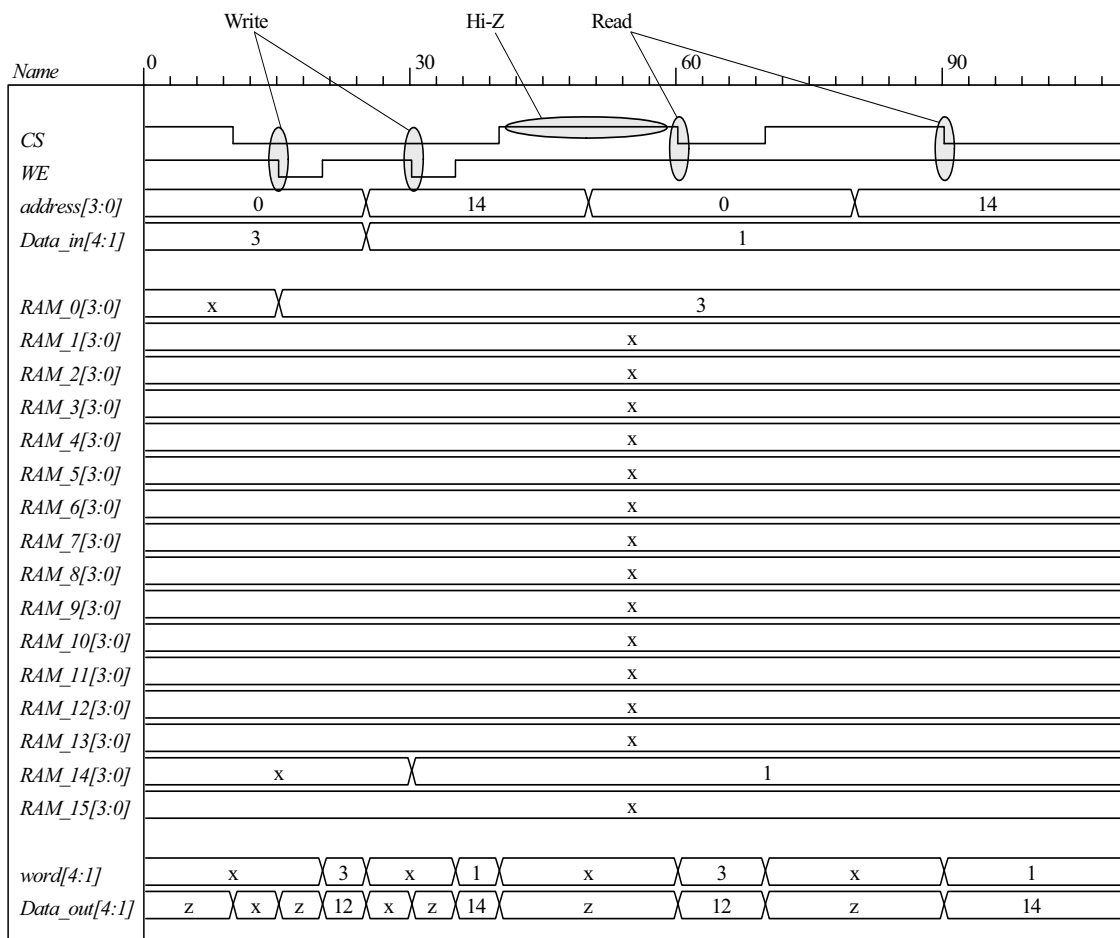
```
initial #110 $finish;  
initial fork  
    WE = 1;  
    CS = 1;  
    address = 0;  
    Data_in = 3;  
    #10 CS = 0;  
    #15 WE = 0;  
    #20 WE = 1;  
    #25 address = 14;  
    #25 Data_in = 1;  
    #30 WE = 0;  
    #35 WE = 1;  
    #40 CS = 1;  
    #50 address = 0;  
    #60 CS = 0;  
    #70 CS = 1;  
    #80 address = 14;  
    #90 CS = 0;  
join  
endmodule
```



Note: Data_out is the complement of the stored value

Supplement to Experiment #14.

```
module Bi_Dir_Shift_Reg_74194 (
    output reg  QA, QB, QC, QD,
    input       A, B, C, D, SIR, SIL, s1, s0, CK, CLR
);
```

```
    always @ (posedge CK, negedge CLR)
        if (!CLR) {QA, QB, QC, QD} <= 4'b0;
        else case ({s1, s0})
            2'b00: {QA, QB, QC, QD} <= {QA, QB, QC, QD};
            2'b01: {QA, QB, QC, QD} <= {SIR, QA, QB, QC};
            2'b10: {QA, QB, QC, QD} <= {QB, QC, QD, SIL};
            2'b11: {QA, QB, QC, QD} <= {A, B, C, D};
        endcase
endmodule
```

```
module t_Bi_Dir_Shift_Reg_74194 ();
    wire QA, QB, QC, QD;
    reg A, B, C, D, SIR, SIL, s1, s0, clock, CLR;
```


```
    Bi_Dir_Shift_Reg_74194 M0 (QA, QB, QC, QD, A, B, C, D, SIR, SIL, s1, s0, clock, CLR);
```

```
    initial #250 $finish;
    initial begin clock = 0; forever #5 clock = ~clock; end
```

```

initial fork
  CLR = 0;
  {A, B, C, D} = 4'hf;
  s1 = 0;
  s0 = 0;
  SIL = 0;
  SIR = 0;
  #10 CLR = 1;
  #30 begin s1 = 1; s0 = 1; end    // load
  #40 s1 = 0;    // shift right
  #100 s1 = 1;   // load
  #110 begin s1 = 0; s0 = 0; end
  #140 s1 = 1;   // shift left
  #160 s1 = 0;   // pause
  #180 s1 = 1;   // resume
join
endmodule

```

 

Supplement to Experiment #16.

The HDL behavioral descriptions of the components in the block diagram of Fig. 11.23 are described in the solutions of previous experiments, along with their test benches and simulations results: 74189 is described in Experiment 13(a); 74157 in Experiment 11(b); 74161 in Experiment 10; 7483 in Experiment 7(a); 74194 in Experiment 14; and 7474 in Experiment 8(a). The structural description of the parallel adder instantiates these components to show how they are interconnected (see the solution to the supplement for Experiment 17 for a similar procedure). A test bench and simulation results for the integrated unit are given below.

```
// LOAD condition for 74194: s1 = 1, s0 = 1
// SHIFT condition: s1 = 0, s0 = 1
// NO CHANGE condition: s1 = 0, s0 = 0
```

```
module Supp_11_16 (
    output [3: 0] accum_sum,
    output carry,
    input [3: 0] Data_in, Addr_in,
    input SIR, SIL, CS, WE, s1, s0, count, Load, select, STB, clock, preset, clear, VCC, GND
);
    wire B4 = Data_in[3]; // Data word to memory
    wire B3 = Data_in[2];
    wire B2 = Data_in[1];
    wire B1 = Data_in[0];
    wire S4, S3, S2, S1;
    wire D4, D3, D2, D1;
    wire S4b = ~S4; // Inverters
    wire S3b = ~S3;
    wire S2b = ~S2;
    wire S1b = ~S1;
    wire D = Addr_in[3]; // For parallel load of address counter
    wire C = Addr_in[2];
    wire B = Addr_in[1];
    wire A = Addr_in[0];
    wire Ocar, Y1, Y2, Y3, Y4, QA, QB, QC, QD, A3, A2, A1, A0;
    assign accum_sum = {D4, D3, D2, D1};

    Flip_flop_7474 M0 (Ocar, carry, clock, preset, clear);
    Adder_7483 M1 (D4, D3, D2, D1, carry, S4b, S3b, S2b, S1b, QD, QC, QB, QA, Ocar, VCC, GND);
    Mux_74157 M2 (Y4, Y3, Y2, Y1, QD, QC, QB, QA, B4, B3, B2, B1, select, STB);
    Counter_74161 M3 (A3, A2, A1, A0, COUNT, D, C, B, A, count, count, Load, clock, clear);
    RAM_74189 M4 (S4, S3, S2, S1, Y4, Y3, Y2, Y1, A3, A2, A1, A0, CS, WE);
    Reg_74194 M5 (QD, QC, QB, QA, D4, D3, D2, D1, Ocar, SIL, s1, s0, clock, clear);
endmodule

module t_Supp_11_16 ();
    wire [3: 0] sum;
    wire carry;
    reg [3: 0] Data_in, Addr_in;
    reg SIR, SIL, CS, WE, s1, s0, count, Load, select, STB, clock, preset, clear;
    supply1 VCC;
    supply0 GND;
    wire [3: 0] RAM_0 = M0.M4.RAM[0];
    wire [3: 0] RAM_1 = M0.M4.RAM[1];
    wire [3: 0] RAM_2 = M0.M4.RAM[2];
    wire [3: 0] RAM_3 = M0.M4.RAM[3];
    wire [3: 0] RAM_4 = M0.M4.RAM[4];
    wire [3: 0] RAM_5 = M0.M4.RAM[5];
    wire [3: 0] RAM_6 = M0.M4.RAM[6];
endmodule
```



```

wire [3: 0] RAM_7 = M0.M4.RAM[7];
wire [3: 0] RAM_8 = M0.M4.RAM[8];
wire [3: 0] RAM_9 = M0.M4.RAM[9];
wire [3: 0] RAM_10 = M0.M4.RAM[10];
wire [3: 0] RAM_11 = M0.M4.RAM[11];
wire [3: 0] RAM_12 = M0.M4.RAM[12];
wire [3: 0] RAM_13 = M0.M4.RAM[13];
wire [3: 0] RAM_14 = M0.M4.RAM[14];
wire [3: 0] RAM_15 = M0.M4.RAM[15];

wire [4: 1] word = {M0.S4b, M0.S3b, M0.S2b, M0.S1b};
wire [4: 1] mux_out = { M0.Y4, M0.Y3, M0.Y2, M0.Y1};
wire [4: 1] Reg_Output = {M0.QD, M0.QC, M0.QB, M0.QA};

```

Supp_11_16 M0 (sum, carry, Data_in, Addr_in, SIR, SIL, CS, WE, s1, s0, count, Load, select, STB, clock, preset, clear, VCC, GND);

```

integer k;
initial #600 $finish;
initial begin clock = 0; forever #5 clock = ~clock; end
initial fork
    #10 begin preset = 1; clear = 0; s1 = 0; s0 = 0; Load = 1; count = 0; CS = 1; WE = 1; STB = 0; end
    // initialize memory
    #10 begin k = 0; repeat (16) begin M0.M4.RAM[k] = 4'hf; k = k + 1; end end
    #20 begin Data_in = 4'hf; Addr_in = 0; select = 1; end
    #30 begin clear = 1; WE = 0; end
    // load memory
    #40 begin
        count = 1;
        CS = 0;
        begin
            repeat (16) @ (negedge clock) Data_in = Data_in + 1;
            count = 0;
            @ (negedge clock) CS = 1;
        end
    end
    #200 count = 1;           // Establish address
    #240 count = 0;
    #250 WE = 1;
    #260 CS = 0;           // Read from memory
    #280 clear = 0;
    #290 clear = 1;
    #300 count = 1;       // Establish address
    #340 begin s1 = 1; s0 = 1; count = 0; end
    #390 CS = 0;
    #400 clear = 0;       // Clear the registers
    #410 clear = 1;
    #420 begin count = 1; CS = 0; end           // Accumulate values
    #490 begin count = 0; CS = 1; end
join
endmodule

```

```

module Flip_flop_7474 (output reg Q, input D, CLK, preset, clear);
    always @ (posedge CLK, negedge preset , negedge clear)
        if (!preset)           Q <= 1'b1;
        else if (!clear)       Q <= 1'b0;
        else                   Q <= D;
endmodule

```

```

module Adder_7483 (
    output S4, S3, S2, S1, C4,
    input A4, A3, A2, A1, B4, B3, B2, B1, C0, VCC, GND
);
// Note: connect VCC and GND to supply1 and supply0 in the test bench
    wire [4: 1] sum;
    wire [4: 1] A = {A4, A3, A2, A1};
    wire [4: 1] B = {B4, B3, B2, B1};
    assign S4 = sum[4];
    assign S3 = sum[3];
    assign S2 = sum[2];
    assign S1 = sum[1];
    assign {C4, sum} = A + B + C0;
endmodule

module Mux_74157 (
    output reg Y1, Y2, Y3, Y4,
    input A1, A2, A3, A4, B1, B2, B3, B4, SEL, STB
);
    wire [4: 1] In_A = {A1, A2, A3, A4};
    wire [4: 1] In_B = {B1, B2, B3, B4};

    always @ (In_A, In_B, SEL, STB)
        if (STB) {Y1, Y2, Y3, Y4} = 4'b0;
        else if (SEL) {Y1, Y2, Y3, Y4} = In_B;
        else {Y1, Y2, Y3, Y4} = In_A;
endmodule

module Counter_74161 (
    output QD, QC, QB, QA,    // Data output
    output COUT,            // Output carry
    input D, C, B, A,       // Data input
    input P, T,             // Active high to count
    L,                      // Active low to load
    CK,                     // Positive edge sensitive
    CLR                     // Active low to clear
);
    reg [3: 0] A_count;
    assign QD = A_count[3];
    assign QC = A_count[2];
    assign QB = A_count[1];
    assign QA = A_count[0];
    assign COUT = ((P == 1) && (T == 1) && (L == 1) && (A_count == 4'b1111));

```

```

always @ (posedge CK, negedge CLR)
if (CLR == 0)          A_count <= 4'b0000;
else if (L == 0)       A_count <= {D, C, B, A};
else if ((P == 1) && (T == 1)) A_count <= A_count + 1'b1;
else                  A_count <= A_count; // redundant statement
endmodule


module RAM_74189 (output S4, S3, S2, S1, input D4, D3, D2, D1, A3, A2, A1, A0, CS, WE);
// Note: active-low CS and WE
wire [3: 0] address = {A3, A2, A1, A0};
reg [3: 0] RAM [0: 15]; // 16 x 4 memory
wire [4: 1] Data_in = { D4, D3, D2, D1}; // Input word
tri [4: 1] Data; // Output data word, three-state output
assign S1 = Data[1]; // Output bits
assign S2 = Data[2];
assign S3 = Data[3];
assign S4 = Data[4];


always @ (Data_in, address, CS, WE) if (~CS && ~WE) RAM[address] = Data_in;
assign Data = (~CS && WE) ? ~RAM[address] : 4'bz; // Note complement of data word
endmodule


module Reg_74194 (
output reg QA, QB, QC, QD,
input A, B, C, D, SIR, SIL, s1, s0, CK, CLR
);
always @ (posedge CK, negedge CLR)
if (!CLR) {QA, QB, QC, QD} <= 4'b0;
else case ({s1, s0})
2'b00: {QA, QB, QC, QD} <= {QA, QB, QC, QD};
2'b01: {QA, QB, QC, QD} <= {SIR, QA, QB, QC};
2'b10: {QA, QB, QC, QD} <= {QB, QC, QD, SIL};
2'b11: {QA, QB, QC, QD} <= {A, B, C, D};
endcase
endmodule

```

 Simulation results: initializing memory to 4'hf, then writing to memory. Note: the values of the inputs are ambiguous until the clear signal is asserted. Signals Ocar and carry are ambiguous because the output of memory is high-z until memory is read is read.



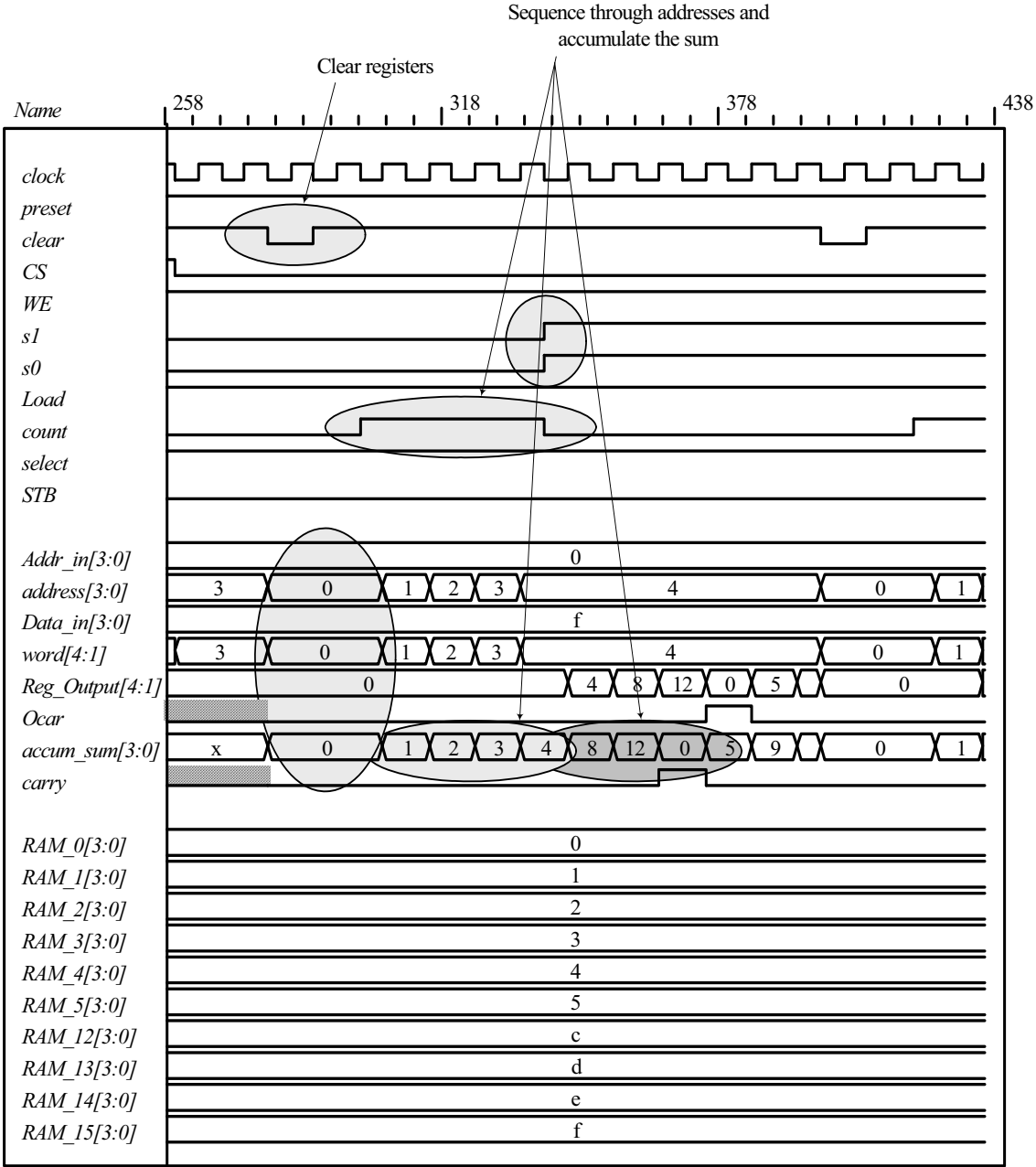

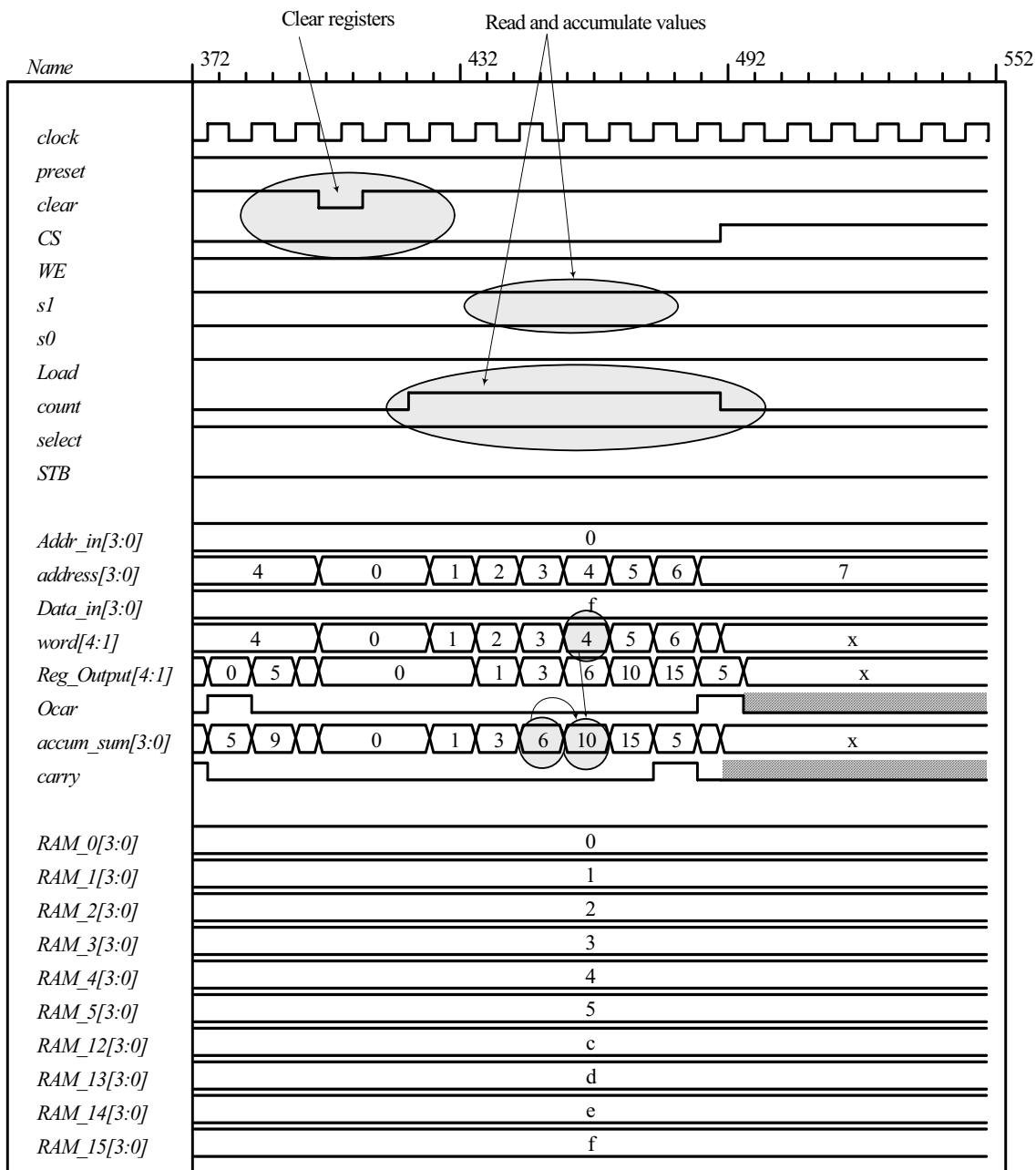

Supplement to Experiment #17.

The HDL behavioral descriptions of the components in the block diagram of Fig. 11.23 are described in the solutions of previous experiments, along with their test benches and simulations results: 74161 in Experiment 10; 7483 in Experiment 7(a); 74194 in Experiment 14; and 7474 in Experiment 8(a). The structural description of the parallel adder instantiates these components to show how they are interconnected (see the solution to the supplement for Experiment 17 for a similar procedure). A test bench and simulation results for the integrated unit are given below.

```
// Control unit is obtained by modifying the solution to Prob. 8.24.
// Datapath is implemented with a structural HDL model and IC components.
// LOAD condition for 74194: s1 = 1, s0 = 1
// SHIFT condition: s1 = 0, s0 = 1
// NO CHANGE condition: s1 = 0, s0 = 0

module Supp_11_17_Par_Mult # (parameter dp_width = 4)
(
    output [2*dp_width - 1: 0] Product,
    output Ready,
    input [dp_width - 1: 0] Multiplicand, Multiplier,
    input Start, clock, reset_b, VCC, GND
);
    wire Load_regs, Incr_P, Add_regs, Shift_regs, Done, Q0;

    Controller M0 (
        Ready, Load_regs, Incr_P, Add_regs, Shift_regs, Start, Done, Q0,
        clock, reset_b);

    Datapath M1(Product, Q0, Done, Multiplicand, Multiplier,
        Start, Load_regs, Incr_P, Add_regs, Shift_regs, clock, reset_b, VCC, GND);
endmodule

module Controller (
    output Ready,
    output reg Load_regs, Incr_P, Add_regs, Shift_regs,
    input Start, Done, Q0, clock, reset_b
);

    parameter S_idle = 3'b001, // one-hot code
               S_add = 3'b010,
               S_shift = 3'b100;

    reg [2: 0] state, next_state; // sized for one-hot
    assign Ready = (state == S_idle);

    always @ (posedge clock, negedge reset_b)
        if (~reset_b) state <= S_idle; else state <= next_state;
    always @ (state, Start, Q0, Done) begin
        next_state = S_idle;
        Load_regs = 0;
        Incr_P = 0;
        Add_regs = 0;
        Shift_regs = 0;
        case (state)
            S_idle: if (Start) begin next_state = S_add; Load_regs = 1; end
            S_add: begin next_state = S_shift; Incr_P = 1; if (Q0) Add_regs = 1; end
            S_shift: begin
                Shift_regs = 1;
                if (Done) next_state = S_idle;
                else next_state = S_add;
            end
            default: next_state = S_idle;
        endcase
    end
endmodule

module Datapath #(parameter dp_width = 4, BC_size = 3) (
    output [2*dp_width - 1: 0] Product, output Q0, output Done,
    input [dp_width - 1: 0] Multiplicand, Multiplier,
    input Start, Load_regs, Incr_P, Add_regs, Shift_regs, clock, clear, VCC, GND
);
```

```

wire C;
wire Cout, Sum3, Sum2, Sum1, Sum0, P3, P2, P1, P0, A3, A2, A1, A0;
wire Q3, Q2, Q1;
wire [dp_width - 1: 0] A = {A3, A2, A1, A0};
wire [dp_width - 1: 0] Q = {Q3, Q2, Q1, Q0};
assign Product = {C, A, Q};
wire [BC_size - 1: 0] P = {P3, P2, P1, P0};

// Registers must be controlled separately to execute add and shift operations correctly.
// LOAD condition for 74194: s1 = 1, s0 = 1
// SHIFT condition: s1 = 0, s0 = 1
// NO CHANGE condition: s1 = 0, s0 = 0

wire B3 = Multiplicand[3];      // Data word to adder
wire B2 = Multiplicand[2];
wire B1 = Multiplicand[1];
wire B0 = Multiplicand[0];
wire Q3_in = Multiplier[3];
wire Q2_in = Multiplier[2];
wire Q1_in = Multiplier[1];
wire Q0_in = Multiplier[0];
assign Done = ({P3, P2, P1, P0} == dp_width);    // Counts bits of multiplier
wire s1A = Load_regs || Add_regs;              // Controls for A register
wire s0A = Load_regs || Add_regs || Shift_regs;
wire s0Q = Load_regs || Shift_regs;            // Controls for Q register
wire s1Q = Load_regs;
wire Pout;                                     // Unused
wire clr_P = clear && ~Load_regs;
Flip_flop_7474 M0_C (C, Cout, clock, VCC, clr_P);
Adder_7483 M1 (Sum3, Sum2, Sum1, Sum0, Cout, A3, A2, A1, A0, B3, B2, B1, B0, GND, VCC, GND);
Counter_74161 M3_P (P3, P2, P1, P0, Pout, GND, GND, GND, GND, Incr_P, Incr_P, VCC, clock,
clr_P);
Reg_74194 M4_A (A3, A2, A1, A0, Sum3, Sum2, Sum1, Sum0, C, GND, s1A, s0A, clock, clr_P);
Reg_74194 M5_Q (Q3, Q2, Q1, Q0, Q3_in, Q2_in, Q1_in, Q0_in, A0, GND, s1Q, s0Q, clock, clear);

endmodule

module t_Supp_11_17_Par_Mult;
parameter dp_width = 4;      // Width of datapath
wire [2 * dp_width - 1: 0] Product;
wire Ready;
reg [dp_width - 1: 0] Multiplicand, Multiplier;
reg Start, clock, reset_b;
integer Exp_Value;
reg Error;
supply0 GND;
supply1 VCC;
Supp_11_17_Par_Mult M0 (Product, Ready, Multiplicand, Multiplier, Start, clock, reset_b, VCC, GND);
wire [dp_width - 1: 0] sum = {M0.M1.Sum3, M0.M1.Sum2, M0.M1.Sum1, M0.M1.Sum0};
initial #115000 $finish;
initial begin clock = 0; #5 forever #5 clock = ~clock; end
initial fork
    reset_b = 1;
    #2 reset_b = 0;
    #3 reset_b = 1;
join
always @ (negedge Start) begin
    Exp_Value = Multiplier * Multiplicand;
    //Exp_Value = Multiplier * Multiplicand + 1;    // Inject error to confirm detection
end

```



```

always @ (posedge Ready) begin
    # 1 Error <= (Exp_Value ^ Product) ;
end
initial begin
    #5 Multiplicand = 0;
    Multiplier = 0;
    repeat (32) #10 begin
        Start = 1;
        #10 Start = 0;
        repeat (32) begin
            Start = 1;
            #10 Start = 0;
            #100 Multiplicand = Multiplicand + 1;
        end
        Multiplier = Multiplier + 1;
    end
end
endmodule

module Flip_flop_7474 (output reg Q, input D, CLK, preset, clear);
    always @ (posedge CLK, negedge preset , negedge clear)
    if (!preset)          Q <= 1'b1;
    else if (!clear)       Q <= 1'b0;
    else                  Q <= D;
endmodule

module Adder_7483 (
    output S4, S3, S2, S1, C4,
    input A4, A3, A2, A1, B4, B3, B2, B1, C0, VCC, GND
);
// Note: connect VCC and GND to supply1 and supply0 in the test bench
wire [4: 1] sum;
wire [4: 1] A = {A4, A3, A2, A1};
wire [4: 1] B = {B4, B3, B2, B1};
assign S4 = sum[4];
assign S3 = sum[3];
assign S2 = sum[2];
assign S1 = sum[1];
assign {C4, sum} = A + B + C0;
endmodule

module Counter_74161 (
    output  QD, QC, QB, QA,    // Data output
    output  COUT,             // Output carry
    input   D, C, B, A,       // Data input
    input   P, T,             // Active high to count
           L,                 // Active low to load
           CK,                // Positive edge sensitive
           CLR                 // Active low to clear
);
reg [3: 0] A_count;
assign QD = A_count[3];
assign QC = A_count[2];
assign QB = A_count[1];
assign QA = A_count[0];
assign COUT = ((P == 1) && (T == 1) && (L == 1) && (A_count == 4'b1111));

```

```


always @ (posedge CK, negedge CLR)
if (CLR == 0)      A_count <= 4'b0000;
else if (L == 0)   A_count <= {D, C, B, A};
else if ((P == 1) && (T == 1)) A_count <= A_count + 1'b1;
else              A_count <= A_count; // redundant statement
endmodule

```

```


module Reg_74194 (
output reg QA, QB, QC, QD,
input A, B, C, D, SIR, SIL, s1, s0, CK, CLR
);
always @ (posedge CK, negedge CLR)
if (!CLR) {QA, QB, QC, QD} <= 4'b0;
else case ({s1, s0})
2'b00: {QA, QB, QC, QD} <= {QA, QB, QC, QD};
2'b01: {QA, QB, QC, QD} <= {SIR, QA, QB, QC};
2'b10: {QA, QB, QC, QD} <= {QB, QC, QD, SIL};
2'b11: {QA, QB, QC, QD} <= {A, B, C, D};
endcase
endmodule

```

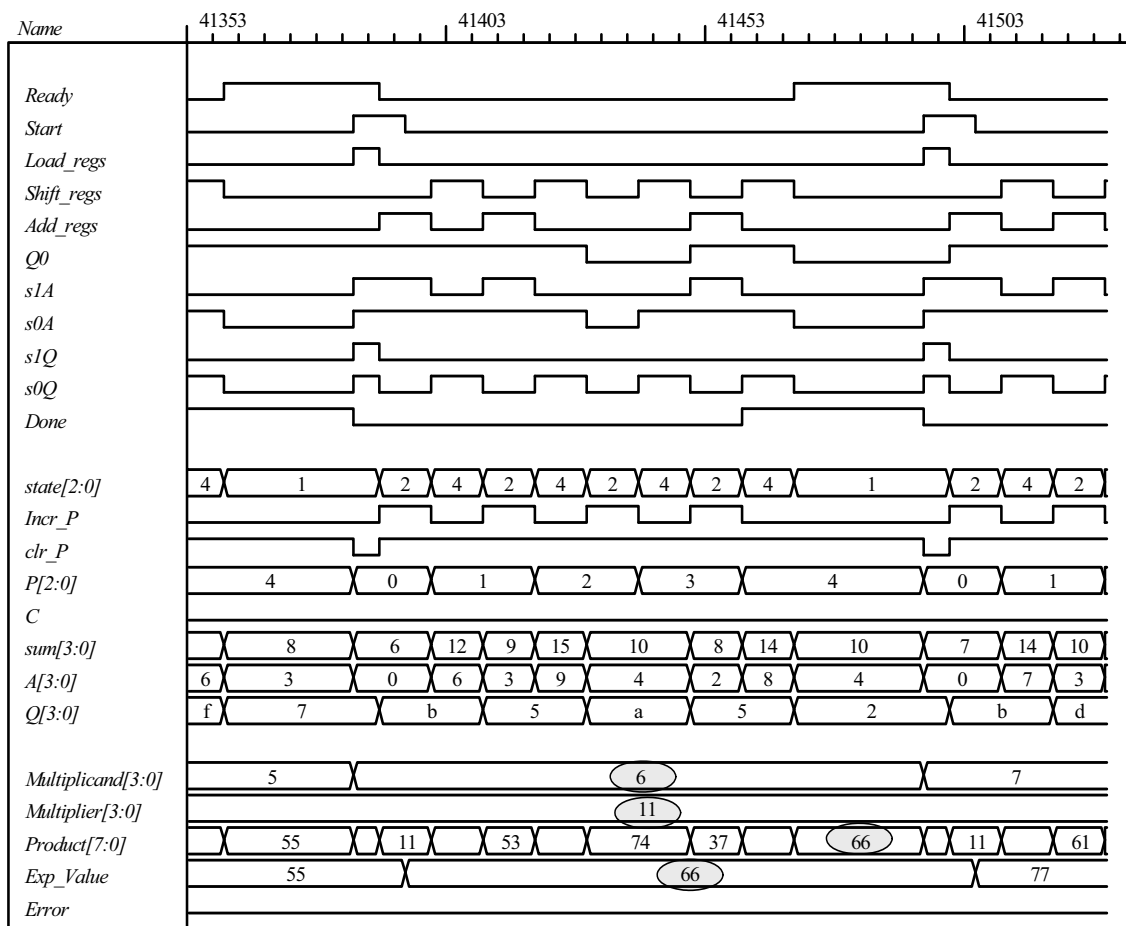


CHAPTER 12

12.1

 


12.2 See textbook.


12.3

 

 
12.4 BCD-to-decimal decoder (similar to IC 7442)




12.5 Similar to 7438:

 

12.6 IC type 74153.

 


12.7

 


12.8 The common control block is used when the circuit has one or more inputs that are common to all lower sections.

12.9

 

12.10 See textbook.

12.11

 

12.12

